

Build this superb 1GHz Digital Frequency Meter

**SILICON
CHIP**


© November, 1987

By STEVE PAYOR

This superb 1GHz Digital Frequency Meter will outperform any other instrument in its price range. It uses the highest performance ICs, provides both frequency and period measurements, and features an 8-digit LED readout.

There is only one way to describe the performance of our new 1GHz Digital Frequency Meter — it's superlative!

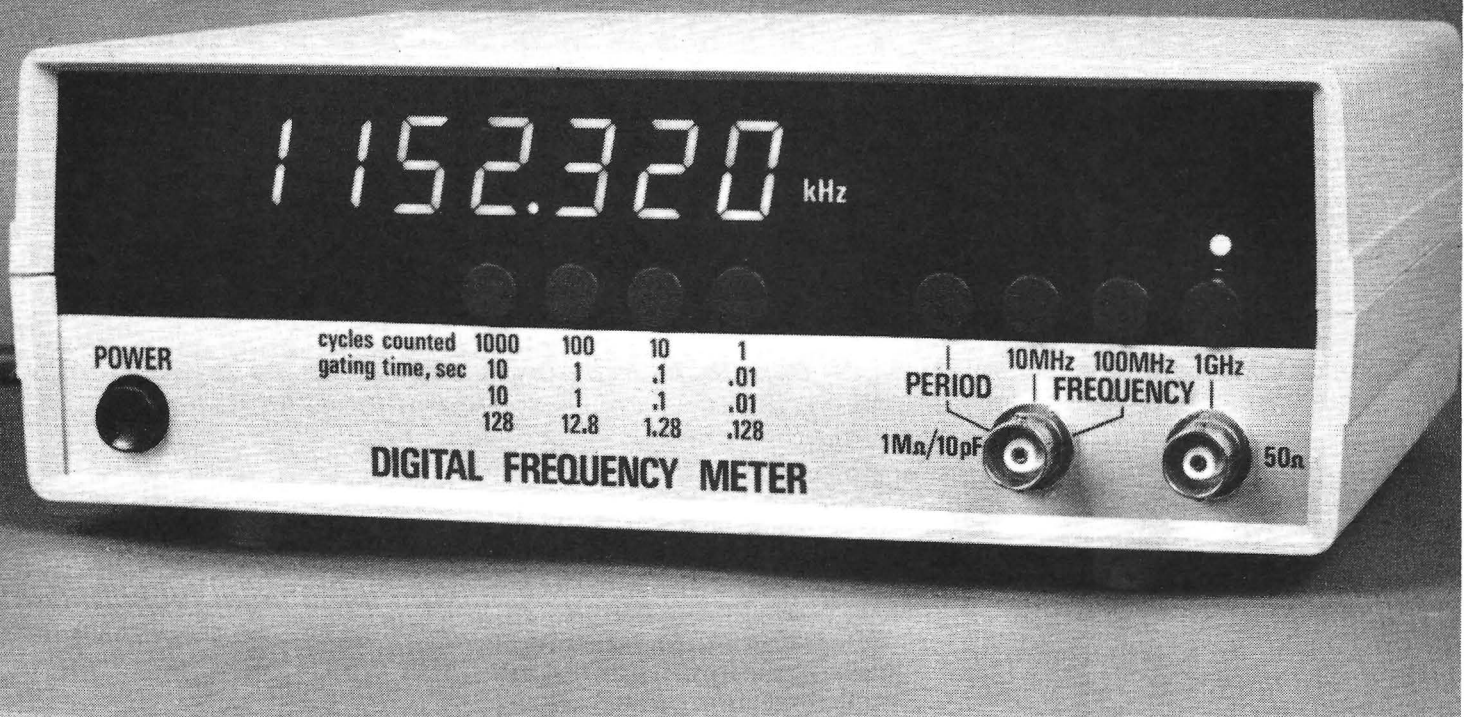The design brief for this instrument was simple: it had to be the best DFM for its price available in Australia. It also had to include both frequency and period measurement modes, a frequency



These two views show the new counter in period mode (left) and frequency mode (right). The unit is housed in an attractive plastic instrument case, with the LED displays hidden behind a red acrylic panel. Note kHz and μ sec indicators.

response to 1GHz, switchable gating times, and an 8-digit readout with switchable decimal points and overflow indication.

And, as if that wasn't enough, the all-up kit price had to be kept to less than \$300!

It took a lot of doing, but we've managed to come up with a very refined design that beats the socks off anything else going. This design not only outperforms existing kit DFMs but also commercial units costing many times more.

To meet our design objectives, we selected three key parts for the circuit: Intersil's ICM7216A LSI frequency counter, Motorola's MC10116 triple differential line driver, and Philips' SAB6456 1GHz divide-by-64 prescaler/amplifier.

The ICM7216A counter IC was chosen because it contains all the circuitry necessary to count, generate gating signals, latch data, and drive an 8-digit multiplexed LED display. It also includes a high-frequency oscillator and control inputs for decimal point placement and gating time.

The 10116 and SAB6456 ICs are used at the inputs of the 0-100MHz and 1GHz ranges respectively. Both are high-speed ECL devices and feature excellent sensitivity across their respective bandwidths — around 20mV in the case of the 10116 and 10mV (max.) for the SAB6456.

The 10116 has been around for a number of years and has been used as a 0-100MHz preamplifier in many commercial DFMs. The SAB6456 is a more recent device, originally designed as a switchable prescaler for use with UHF/VHF television tuners. It has a guaranteed range of operation from 70-1000MHz.

Three other ECL devices have also been used in the circuit: two 10131 dual-D flipflops which have been configured as divide-by-five and divide-by-two counters, and a 10100 three input NOR gate.

Finally, a few inexpensive CMOS chips round out the IC count in our new DFM. These devices are used for frequency division and logic switching.

Main features

Let's take a look at some of the features of the unit.

As seen from the front of the instrument, there are two groups of four pushbuttons: the RANGE buttons, which move the position of the decimal point, and the FUNCTION buttons which select the various period and frequency modes. Throughout the following circuit description, these buttons will be referred to as R1, R2, R3, R4 and F1, F2, F3 and F4 respectively.

The RANGE buttons select the gating time when in frequency mode, and the number of cycles counted when in period mode.

The FUNCTION buttons select the various operating modes: either period or three frequency ranges (0-10MHz, 0-100MHz or 10MHz-1GHz). Immediately below these pushbuttons are two BNC input sockets. One of these has an input impedance of 1M Ω shunted by 10pF and is used for period and frequency measurements up to 100MHz.

The second input has an input im-

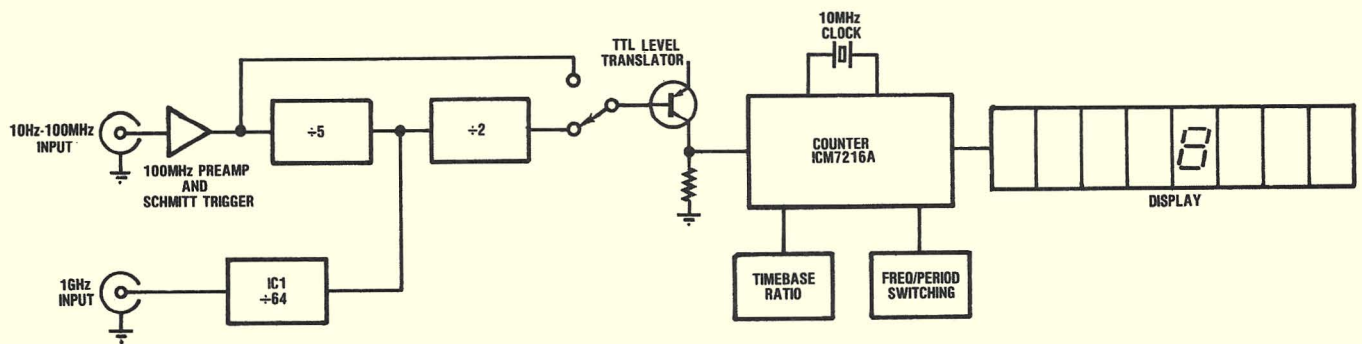


Fig.1: this diagram shows the main circuit blocks of the counter. Signals applied to the 10Hz-100MHz input are amplified, and divided by 10 or fed direct to the base of a TTL level translator (Q2). Similarly, signals applied to the 1GHz input are divided by 128 before reaching Q2. Q2, in turn, clocks an Intersil ICM7216A counter IC which drives the LED display.

pedance of 50Ω and is used for frequency measurements up to one gigahertz (1GHz).

An interesting feature of the unit is the provision of four switchable gating times: .01, 0.1, 1 and 10 seconds for the 10Hz to 100MHz input, and 0.128, 1.28, 12.8 and 128 seconds for the 1GHz input.

The gating time is simply the time over which measurements are made before the display is updated. A long gating time means a higher count and greater resolution, but the drawback is slow update times.

Selectable gating times thus make for a more versatile unit. You can opt for high resolution or fast update time, or a compromise between the two, as the situation demands.

In the period mode, the gating switches select the number of cycles counted before the reading is displayed — either 1, 10, 100 or 1000. This mode allows very accurate measurement of low frequency signals (ie, those below about 10kHz). As before, you can opt for high resolution, fast update time, or a compromise between the two.

All readings are displayed directly in kilohertz (kHz) or microseconds (μsec), depending on the mode selected. As you can see from the photographs, the display features both kHz and μsec indicators, together with LED indication of the mode selected. Another LED, situated in the top left-hand corner of the display, provides overflow indication.

Easy to build

We've put a lot of work into making this unit easy to build so that the specs of your assembled kit will match those of the prototype.

All parts, with the exception of the power supply components, are mounted on two printed circuit boards which are soldered together at rightangles by means of matching solder pads. A red acrylic panel fitted with a Scotchcal label is attached to the display PCB by means of the BNC input sockets. The whole assembly then slides into matching grooves in a compact plastic instrument box.

A third PCB accommodates the power supply components and is mounted together with the transformer, on the rear panel. We did this so that heat-generating components, such as the power transformer and a voltage regulator IC, were as far away from the sensitive counter circuitry as possible.

Circuit description

Before getting down to details, it is interesting to note that only two logic families are used in this frequency meter: the aforementioned ECL (Emitter Coupled Logic) for the high-speed "front end" circuitry, and CMOS for the remainder. All the ICs are common types except for the 1GHz ECL prescaler (Philips SAB6456) and the main CMOS counter/display driver (Intersil ICM7216A).

Another interesting feature is the

complete elimination of front-panel wiring. This was made possible by using PCB-mounted pushbutton switches and by electronically switching signal paths. Normally, one would expect to see a bank of mechanically latched and interlocked pushbuttons, but here the mechanics have been replaced by CMOS logic circuitry.

Viewed as a whole, the circuit is quite a jigsaw puzzle, so we will examine it one section at a time, starting with the inputs.

The 0-100MHz input

This input is used for period measurements to 0.4μs (2.5MHz) when function button F1 is pressed, and frequency measurements up to 100MHz. The input impedance is nominally 1MΩ with protection against all but the worst overloads.

Firstly, any DC component of the signal is removed by the 0.047μF input coupling capacitor. The signal is then clipped by a pair of BAW62 high-speed silicon diodes in conjunction with a series 180kΩ current-limiting resistor. Note: do not substitute other types here as these diodes have exceptionally low capacitance (1pF typ.) and a high current rating.

To maintain a flat frequency response, the 180kΩ resistor is shunted by an 18pF capacitor (C1) which compensates for the stray capacitance to ground across the 820kΩ resistor of about 4-5pF (due to the diodes and JFET Q1).

A JFET source-follower (Q1) is us-

ed to buffer the input signal, and the voltage gain of this stage is about 0.7. Not shown on the circuit diagram, but connected to the source of the JFET, is a small "guard" track which surrounds the input circuitry on the PCB. This helps to minimise the stray capacitance around the input components, and the net result is an effective circuit input capacitance of only 6pF.

In practice, by the time we add an input socket and plug, it is closer to 10pF.

100MHz preamp

This part of the circuit amplifies the incoming signal and converts it to a "clean" square wave suitable for the logic and counting circuitry.

At first glance, the requirements of high gain and a frequency response flat to 100MHz may seem

a little daunting, but this is achieved with a standard ECL differential line receiver (10116) and careful circuit layout.

Note: readers unfamiliar with the internal circuitry of ECL should refer to the accompanying panel.

The 10116 contains three differential amplifiers, each with complementary outputs. Also provided is a DC bias voltage, V_{BB} (pin 11), which we have used to bias the inputs of the first stage (IC2b).

The signal is capacitively coupled from the JFET buffer stage and, by keeping as much symmetry in the layout as possible, most of the noise picked up at this point is effectively cancelled by the balanced differential input. This is important because the proximity of the 8-digit multiplexed LED display makes for a very noisy environment.

The DC balance of the first stage is adjusted by VR1. Since each in-

put draws approximately $13\mu A$ of bias current, this $1k\Omega$ multi-turn trimpot can shift the DC input voltage by $\pm 13mV$.

The voltage gain of the first stage is about seven.

The second stage (IC2c) has some negative feedback to reduce its gain. This feedback is applied from one output to its corresponding inverting input by two 100Ω resistors. If IC2c was an operational amplifier, it would have a gain of -1 via the inverting input and $+2$ via the non-inverting input, giving a total differential gain of three. But since the open loop gain is only seven (instead of practically infinity in the case of an op amp), the actual stage gain is closer to two.

There are reasons for reducing the gain here. First, using all the available gain would make the circuit too sensitive. To give a good stable reading, a DFM must be able

All About Emitter Coupled Logic

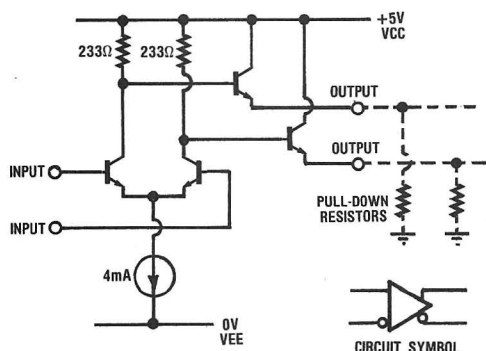


Fig. 2 BASIC ECL DIFFERENTIAL AMPLIFIER

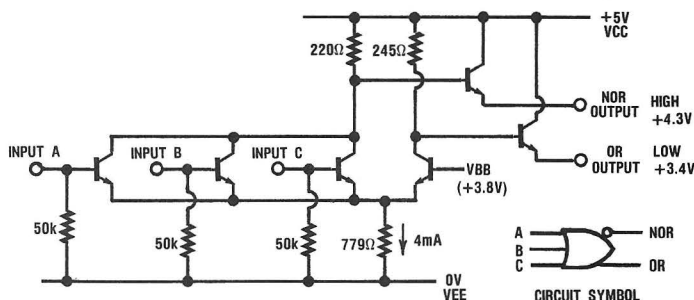


Fig. 3 BASIC ECL LOGIC GATE

Emitter Coupled Logic (ECL) was one of the first forms of bipolar logic to be produced as monolithic integrated circuits, back in the early 1960s. Today, it is still the fastest form of logic available, with propagation delays of less than one nanosecond per gate quite common.

The ECL 10,000 series ICs used in this project are slowed internally to make them less critical to use with normal circuit wiring. The propagation delay is 2ns and the rise and fall times have been slowed to 3.5ns.

ECL ICs are normally designed to run from a $-5.2V$ supply (V_{EE}),

but they also work quite well from a $+5V$ supply; ie, $V_{CC} = +5V$ and $V_{EE} = 0V$.

Fig.2 shows the basic structure of an ECL differential amplifier. Depending upon which input is at the higher voltage, either the left or the righthand transistor in the differential pair will be turned on and the voltage across its collector load will be about 0.9V while the collector of the other transistor will be at V_{CC} . Each collector output is buffered by an emitter follower, which gives an output voltage swing between $+3.4V$ (logic low) and $+4.3V$ (logic high).

An external pull-down resistor is

required on each used output.

Fig.3 shows how this basic structure is modified to form a logic gate. A number of transistors (one for each input) are connected in parallel on one side of the differential circuit, while the transistor on the other side is connected to an internally generated bias voltage (V_{BB}) which is half-way between the high and low logic levels; ie, about $+3.8V$. When one or more of the inputs is taken above $+3.8V$, the current shifts from the right to the left hand side of the emitter-coupled circuit and the NOR output goes low, while the OR output goes high.

FOR NEXT DAY JETSERVICE DELIVERY



Altronics Will Deliver Any Of These Quality Products To Your Door Faster Than Any Other Australian Supplier Or Your Money Back

(Within 24 Hours To Every Capital City and Suburbs - Allow Additional 24 - 48 Hours For Country Areas)

SAVE \$\$\$ SAVE \$\$\$ Great Little PA Amplifier

This natty little amplifier includes some remarkable features which, until now have only been available on very expensive commercial items e.g. Balanced Mic Input - This enables you to run very long microphone leads without troublesome interference or hum pickup. **Balanced line output** - This enables you to run the speaker lines right alongside the microphone line without instability. **Constant voltage design** allows you to switch on one speaker circuit or all circuits together without any noticeable variance in output sound level.

Output Power is a genuine 30 watts into either 100V line or 4 Ohms.

A 2000 **\$259**




Super Compact Transformer
Delivers 12, 15, 24, 27, 30V
At Up to 10 Amps
Just The Shot for 12 & 24V
Supplies & Charging;
Circuits

Multipurpose 120VA Transformer

Another Quality Transformer from Altronics. The M 2175 is wound on expensive grain oriented steel. Look at the size! Just 110mm Wide by 65mm High by 65mm Wide. Weight 1.25Kgs. M 2175

Primary 240V
Secondary 1 0—12V @ 5A, 15V @ 4A
Secondary 2 0—12V @ 5A, 15V @ 4A

1—9 **\$39.95** 10Up **\$35.00ea**

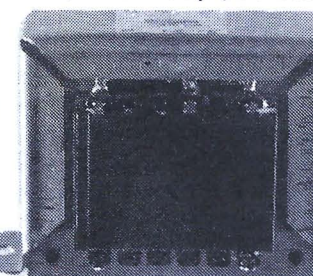

Solder
200g Reel
\$7ea

10 or More **\$6**



T 1200

20MHz Logic Probe

Input Z 1M Ohm. TTL Logic Hi LED greater than 2-3V. Logic 0 Lo LED Less than 30% Vcc. Min Detectable pulse width 30 nSec. Cat. Q 1272


\$29.95



Horn Relay

12-16V coil 20 Amp
Contacts S 4130

1/2 Price **\$3.75**

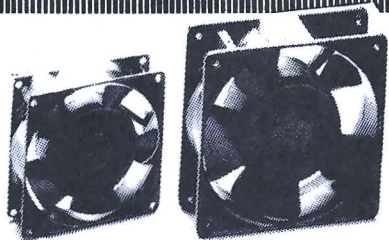

Rugged Ultra Quiet- Now With Metal Diecast Frame

240V High Specification Computer Fans

Durable Die Cast Aluminium Venturi PBT Plastic impeller of 94V—0 material. Shaded pole motor.

80mm x 80mm x 32mm

Air Flow 45 C.F.M. Input Power 16W Speed 2300 RPM Noise Level 31 dba. Cat. F 1020

\$24.50ea 4 or More **\$22.50**

120mm x 120 x 38mm

Air Flow 80C.F.M. Input Power 25W Speed 2600 RPM Noise Level 43 dba. Cat. F 1030

\$24.50ea 4 or More **\$22.50**



Fan Finger Guards

F 1022 (for 80mm Fan) **\$1.50**

F 1032 (for 110mm Fan) **\$1.50**

10 Watt Twin Cone Speaker 8" (200mm)

Great for PA, Background Music and HiFi extension use. Over 90,000 sold in Australia. Cat. C 2000

1-9 **\$12.95**

10 Up **\$11.00ea**



150W HiFi-PA Piezo

144.8 x 54mm Rectangular Piezo Horn Speaker suitable for HiFi and Sound Reinforcement. Full 90 deg. horizontal dispersion angle • Freq.Res. 3 to 40KHz • S-1s: 110db @ 2.8V Cat. C 6120

\$18.95 4 Up **\$17**



Toroidal Power Transformers

Why a Toroid?

• Smaller size and weight to meet modern "slimline" requirements • Low electrically induced noise demanded by compact equipment • High efficiency enabling conservative rating whilst maintaining size advantages. • Lower operating temperature • Simple, quick single bolt mounting.

160 Watt Models

Cat.No.	SEC.V
M 3050	12 + 12
M 3055	18 + 18
M 3060	25 + 25
M 3065	30 + 30
M 3070	35 + 35
M 3075	40 + 40
M 3080	45 + 45

\$59.95ea

5 Up **\$55.00ea**


300 Watt Models

Cat.No.	SEC.V
M 3085	12 + 12
M 3086	18 + 18
M 3088	25 + 25
M 3090	30 + 30
M 3092	35 + 35
M 3100	40 + 40
M 3105	45 + 45

\$69.95ea

5 Up **\$65.00ea**

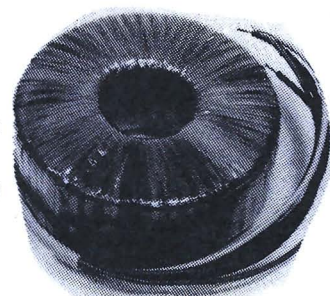These are the Genuine English TOROIDS as Specified in various Electronics Australia Projects



Dimensions & Weight

160 VA Models 110 Diam. 45mm H. 1.8Kgs. Leads 200mm
300 VA Models 125 Diam. 45mm H. 2.5Kgs. Leads 200mm

Engineers Multimeter

\$10 Off This Month

Includes Continuity Buzzer

20,000 Ohms/Volt DC • 8,000 Ohms/Volts AC. Mirror backed scale • Overload protected. 10 amp DC current range. Unique carry handle doubles as a bench stand.

RANGES

DC Voltage
2.5, 10, 50, 250, 1000V
AC Voltage
10, 50, 250, 1000V
Decibels
—8db to +62db
DC Current
5, 50, 500mA


Ohm meter 0-6 meg.
Ohms in 3 ranges, 50 Ohms centre scale.
Size 135 x 91 x 39 mm

Includes Battery Tester

Q 1018

Normally **\$39.95**

Now **\$29.95**

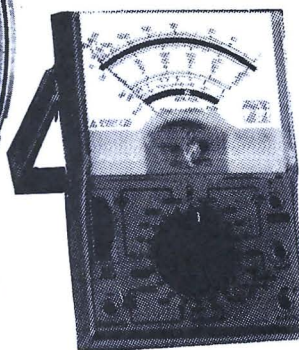


Why Risk Unnecessary Heart Attack?

Heart disease strikes down many people in their early 40's (or even 30's). The tragedy remains that had such victims been alerted, remedial medical, physical and dietary action could have been prescribed to avoid illness and in many cases restore full bodily health. X 3055

Blood Pressure and Heart Rate Monitor

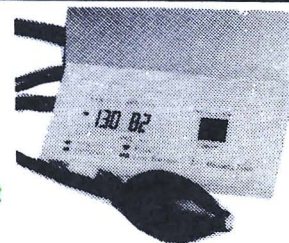Features:
• Non-Microphone Measurement System
• LCD Readout
• Blood Pressure Monitor
• Pulse Rate Monitor




Why Pay \$150?

X 3055 Only **\$110**

FOR NEXT DAY JETSERVICE DELIVERY

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008 999 007 FOR NEXT DAY JETSERVICE DELIVERY

LOOK Great Projects To Build

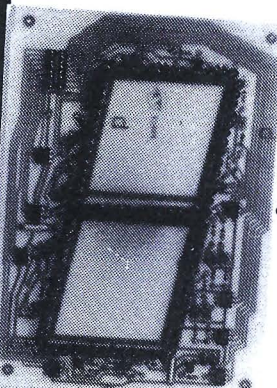

Fantastic New Kit From EA
Super Large LED Display Module
 (Display 150 x 60)

Need to produce an LED display that can be seen from a long way off? This single digit 153mm high seven segment LED display module is just what you need. It can be used as a replacement for both common anode and common cathode LED displays, can be either multiplexed or DC driven, and can be provided with a decimal point on either the right or left.

External DC Supply Required 20 - 24V at 150mA

K 1225 **\$49.95**


This Natty Single Button Security Lock Is Just The Shot For Your Garage, Workshop, Wine Cellar Or Front Door

4-Digit Combination Lock

This electronic combination lock has a four digit security code which is entered using a single pushbutton switch. For added security, each number of the code must be entered within certain time restraints. Once the correct code has been entered, the circuit triggers a solenoid operated door catch to unlock the door.

Altronic Kit Housed in sturdy Jiffy Box.

K 1925 **\$35.00**

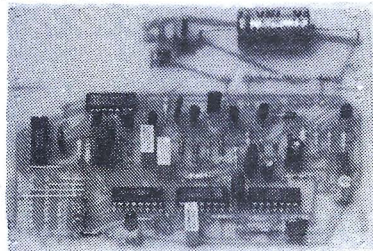


Excludes Solenoid Door Catch (Available from your local Security Store)

TRANSISTOR ASSISTED IGNITION WITH DWELL EXTENSION

Dead easy to build and (even better) there are only 3 electrical connections required to the car wiring system.

K 4010 **\$39.50**

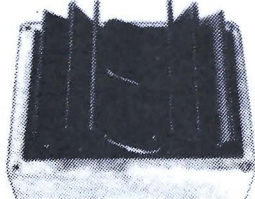

The Power House Arrives

Massive 600 Watt Inverter

Operates from 12 or 24 Volt systems via internal wiring connections

Big brother to our 300W Model this brilliant design can be internally connected for either 12 or 24V operation. Full 600 watt output — and that will power a fantastic array of appliances e.g. Lighting, Electric Motors, Electric drills, Hi Fi, TV Sets, Computer. An absolute must for House Power or for the Truck, Tractor etc.

K 6770 Complete Kit **\$399.00**
 K 6775 Fully Built & Tested **\$499.00**



With Soldering Stations Costing \$150 and More, This Represents Excellent Value

Temperature Controlled Soldering Station

(EA Sept. '88)

Controls the temperature of your standard soldering iron. Suitable for irons rated from 20W—75W - Standard soldering iron plugs straight in, no need for modification.

The Altronic Kit comes complete — Pre-punched and silk screened. K 6400

\$35.00



Zener Tester
 Used with your multimeter - Reads exact zener voltage up to 60V. K 2620
\$12.50

Save A Bundle On Those Dangerous Pesticides

Build EA's Great Ultrasonic Pest Repeller


EA's "Pest Off" generates frequencies between 23KHz and 64KHz claimed to be the best for driving off most vermin and beasts. K 1600



\$39.95

Blowing Fuses Blowing Your Cool? You Need The Electronic Fuse

K 2535 **\$32.50**

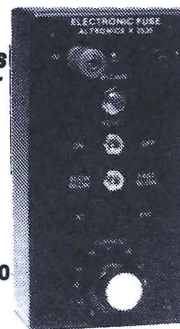

All you do is clip the unit across the DC fuse holder (fuse removed), dial up the required current (max. 10A) and if the circuit draws more than this then the circuit "trips" or opens. Thus power is removed from the device.

Features: Fast blow - slow blow setting • Manual reset button • LED fuse tripped indicator • Operates off 1 single 9V battery (not supplied) • Two current ranges 0-1A & 0-10A • Any current setting available up to 10A • Current Settings easily adjustable via a pot and calibrated scale. • Housed in a rugged Jiffy Box.

A Must for prototyping and service work. No Electronic workshop should be without one.

Video Enhancer

Sharpens up your picture when Copying Video to Video



\$42.50

Here's a simple but effective video enhancer that is super easy to build at a fraction of the cost of commercial models. Unit sharpens picture detail, and can actually improve the quality of a copy by amplifying the top end of the video signal K 5825

Screacher Car Burglar Alarm

This alarm drives off wouldbe thieves with an ear splitting modulated tone. Once activated it is near impossible to stay within the confines of the car.

Features: Entry Delay • Exit Delay • Alarm Timer • Lamp Flasher • Three second soft alarm reminder. Piezo siren produces modulated tone of 110db at 1 metre. Simple to build and install. Two Sensor inputs

Ultrasonic Movement Detector


This Ultrasonic Movement Detector provides added protection against illegal entry via an open window etc. Connects directly to an alarm with a normally open input. Detects any movement up to 3 metres within an angle of 30 degrees. Will operate directly off 12V i.e. Car Battery etc.



K 4400 **\$29.50**

Mosfet Power Amp Module 150 Watt

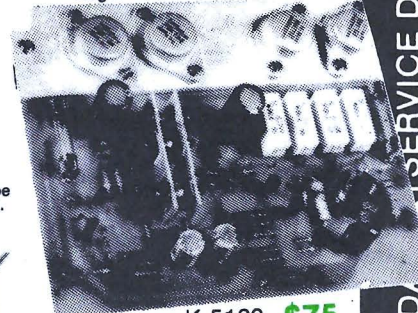Here is a high power, general purpose power Amplifier module suitable for HiFi, guitar and PA applications employing sturdy, reliable MOSFET's in the output stage.



K 5120 **\$75**

SPECIFICATIONS:

Power Output
 150W RMS into 4 Ohms
 100W RMS into 8 Ohms
 (At onset of clipping)
Frequency Response
 20Hz to 20KHz +0 -0.5db
 10Hz to 60KHz +0 -3db
 (Measured at 1 W and 100W Levels)
Input Sensitivity
 1 Volt RMS for full output

Hum
 98db below full output

Noise
 114db below full output

Total Harmonic Distortion
 0.006% @ 1KHz 12W
 0.03% @ 10KHz 12W


Stability
 Exceptional (tested to full output driving 3.3uF into short circuit at 10KHz).



DIGITAL PHOTO TIMER \$79.50

This classy digital timer allows precision timing for photographic processing from 1 second up to 9 minutes 59 seconds in 1 second increments.

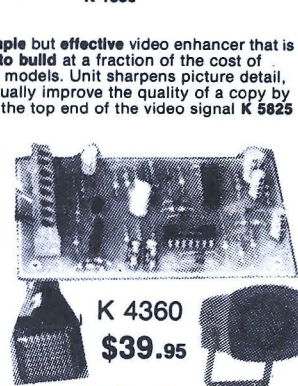Features: Large easy to read LED displays. Hold switch which interrupts timing and focus switch which bypasses the timer settings. K 1850



K 4360 **\$39.95**

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008 999 007 FOR NEXT DAY JETSERVICE DELIVERY


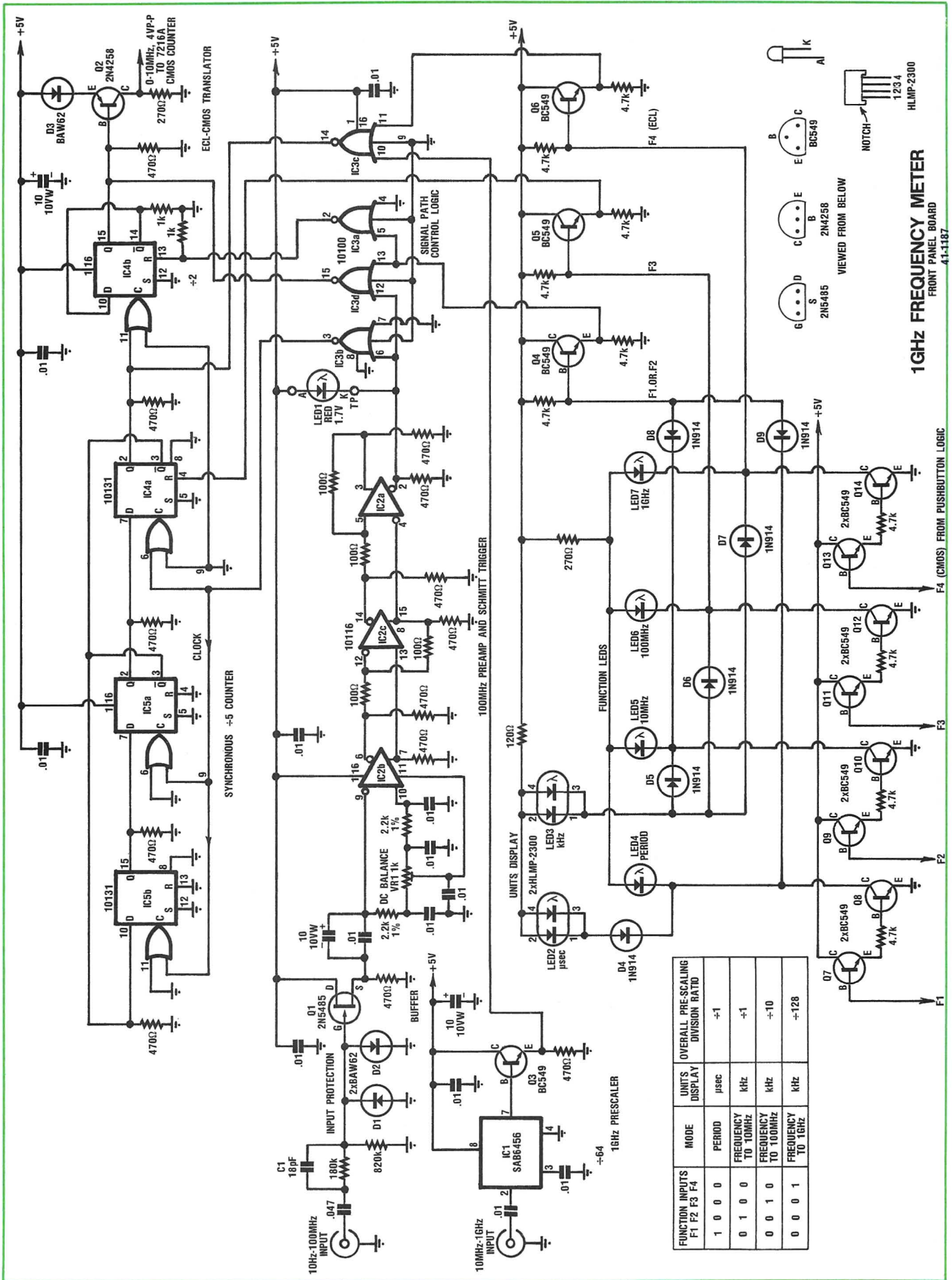


Fig. 4: the front panel circuitry. Signals from the 100MHz preamp (IC2) and 1GHz prescaler circuits (IC1) are fed to NOR gate IC3. The signals are then divided by counter stages IC4 and IC5, or fed direct to the base of level translator Q2.

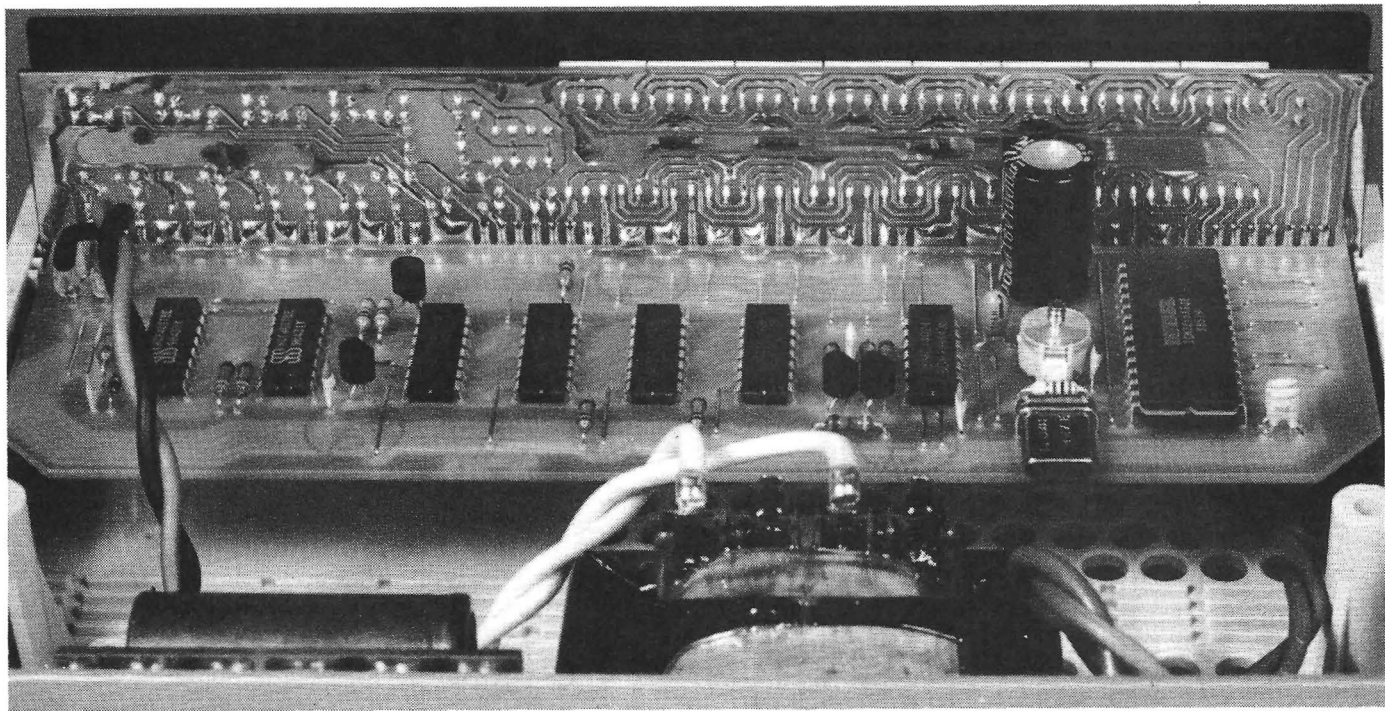

Most of the counter circuitry is mounted on two PCBs which are soldered together at rightangles. This view shows the parts on the main counter PCB. The Intersil ICM7216A is at the right.

to ignore the noise which is always present on the signal. The sensitivity we have chosen is about optimum for most audio and RF measurements without the need for an input attenuator.

The second reason for using negative feedback has to do with maintaining the high-frequency performance, which will be discussed a little later.

The third stage, IC2a, may appear similar to the second stage, but in this case the feedback is positive rather than negative. This means that IC2a functions as a Schmitt trigger rather than as a linear amplifier.

The positive feedback around IC2a causes it to latch in either the 1 or 0 state when no signal is present. To toggle the output, the signal amplitude must exceed the hysteresis voltage which is about 450mV.

By working backwards from the here, we can calculate the theoretical sensitivity of the instrument; ie. 450mV divided by 2 (second stage gain) divided by 7 (first stage gain) divided by 0.7 (JFET buffer) divided by 0.82 (input protection) = 56mV p-p, or 20mV RMS.

Any noise signal with an amplitude of less than 56mV peak-to-

peak will thus be ignored.

At frequencies above 50MHz, the sensitivity of the Schmitt trigger is degraded somewhat by the phase shift (propagation delay) within the ECL amplifier. Thus, the positive feedback becomes less positive. At the same time, the negative feedback around the previous stage becomes equally less negative; ie. the gain of the second stage actually increases slightly.

The serendipitous result is a relatively constant sensitivity up to around 100MHz, without the need for small "peaking" capacitors across the feedback resistors.

Fig.6 shows the measured performance of one of the prototypes. The sensitivity was better than 20mV RMS over most of the frequency range, rising to around 90mV at 140MHz. The small "bumps" at 50Hz and 500Hz were caused by internal noise — from mains hum and the multiplexed digital display respectively.

This noise slightly degrades the theoretical noise immunity, reducing the maximum amount of "ignorable" noise at the input socket from 56mV p-p to about 30mV p-p.

A test point is provided at the output of IC2a for setting up and

testing the above circuitry. The state of the Schmitt trigger can be monitored by plugging a 1.7V red LED into a pair of Molex pins on the PCB. The number of turns of trimpot VR1 required to turn the LED on or off provides a convenient check of circuit operation.

Following IC2a, the now digital signal is routed to the base of TTL level translator Q2 via one of two paths: either directly via ECL OR gate IC3d when F1 or F2 is selected, or via IC3b and a high-speed divide-by-10 counter when function F3 is selected.

The 1GHz input

This input is used for frequency measurements from 10MHz to above 1GHz, and is selected by pressing function button F4.

Surprisingly, this is one of the simplest parts of the circuit, thanks to the use of a Philips SAB6456 UHF prescaler (IC1). As mentioned above, this IC is normally intended for use in TV tuners where its function is to divide down the frequency of the local oscillator, as part of a frequency synthesiser circuit. Because it is designed to be driven by small-amplitude sinusoidal signals over a wide frequency range, it is ideal for our application.

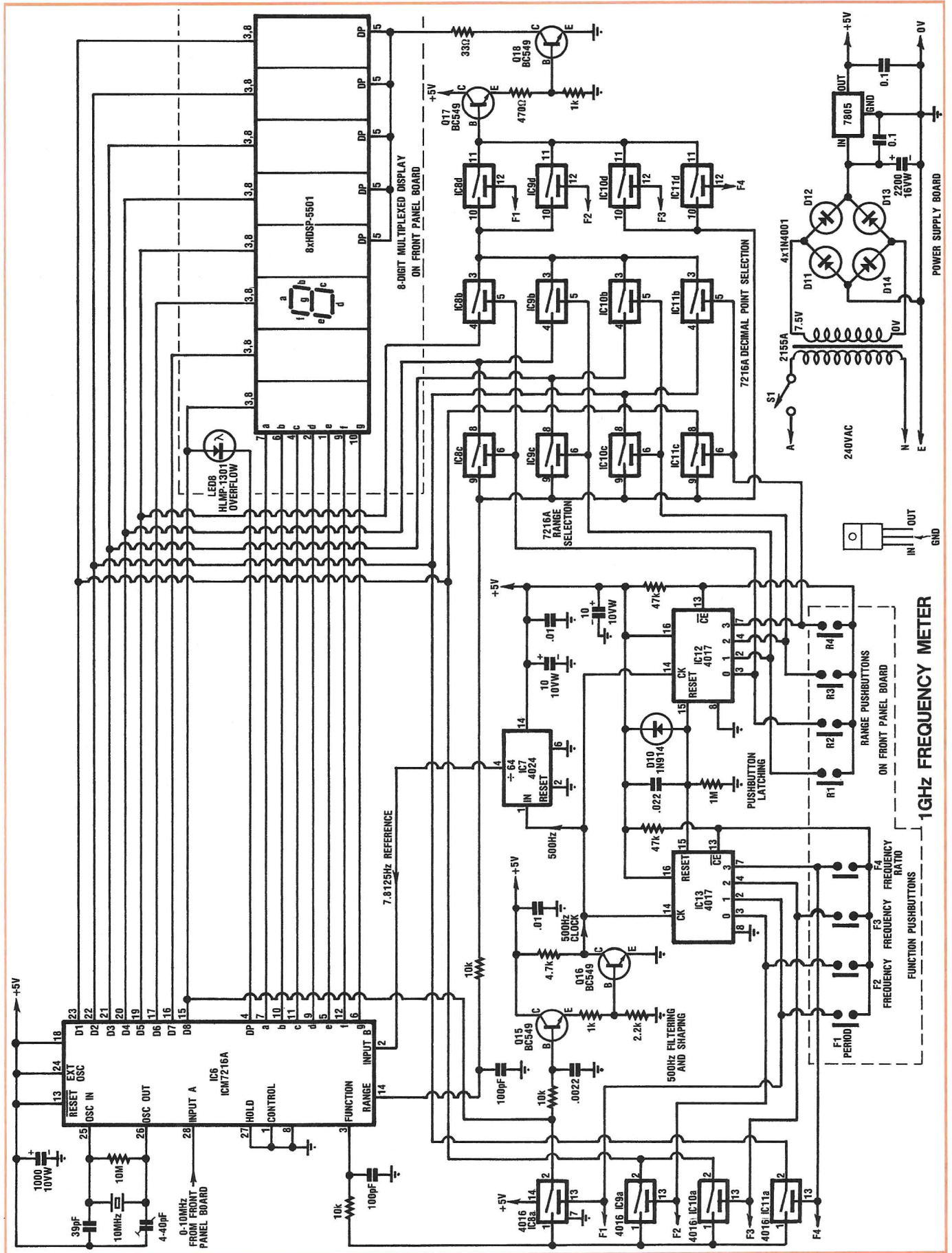


Fig.5: diagram showing the counter, display and power supply circuitry. Also shown is the latching circuitry for the function and range pushbuttons (IC8-12). This section will be described next month.

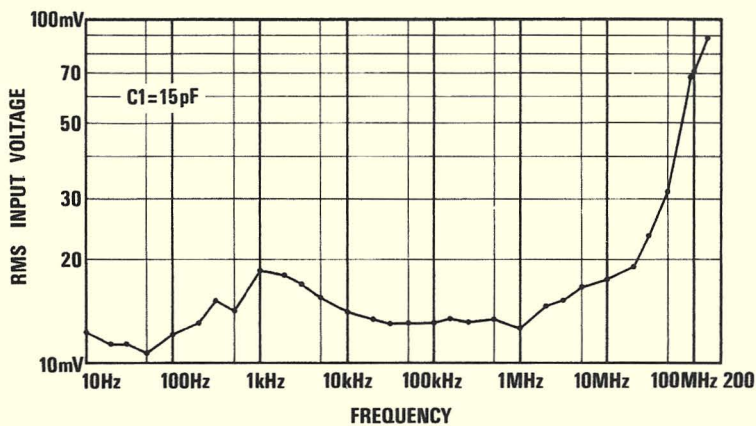


Fig.6: the measured sensitivity of the prototype was better than 20mV RMS over most of the range, rising to about 90mV at 140MHz.

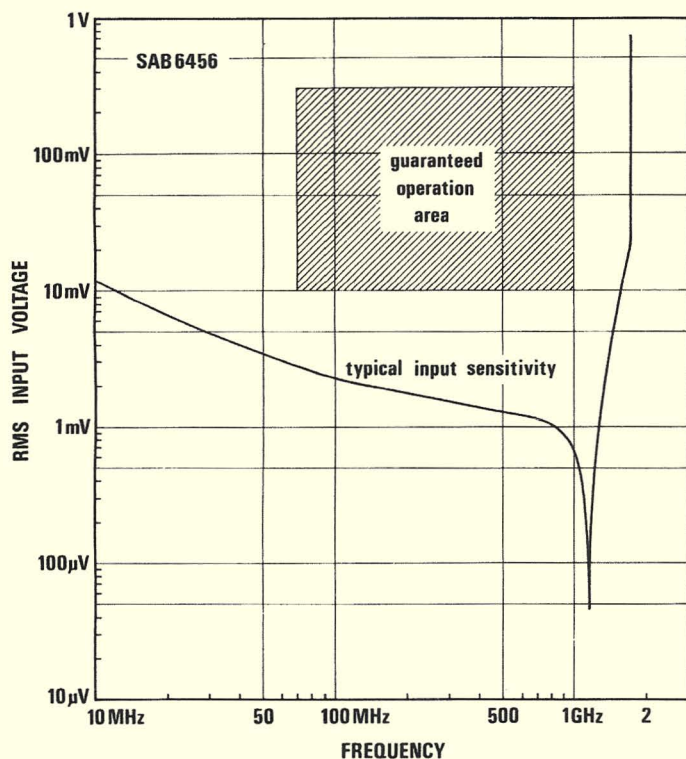


Fig.7: the SAB6456 has a guaranteed range of operation from 70-100MHz with a sensitivity of 10mV. Actual devices have a cutoff frequency of typically 1.7GHz.

Pins 2 and 3 are differential ECL inputs, which are biased internally, so that the only external parts needed are two input coupling capacitors. These capacitors should ideally be leadless ceramic "chip" types, since the inductance of the leads on ordinary ceramic capacitors can be a problem at 1GHz. However, we have found that Philips miniature ceramic plate

capacitors (2222-629 series) are useable, provided they are seated right down on the PCB, with an absolute minimum of lead length.

Note: this applies to all the 0.01µF ceramic capacitors used throughout the circuit for high-frequency coupling and bypassing.

No overload protection is provided on the 1GHz input since the usual pair of back-to-back diodes

would provide too much of a capacitive load at 1GHz. In any case, most applications will not require a solid connection to this input. The sensitivity is very high, and according to the manufacturer's specifications, is guaranteed to be better than 10mV RMS from 70MHz to 1GHz (Fig.7).

The typical input sensitivity at 1.2GHz is, in fact, a mere 50µV RMS, and the input will usually oscillate at this frequency when no signal is applied. In practice, this is of no consequence since the prescaler will stop oscillating when a valid signal is present. In fact, this self-oscillation provides us with a convenient way of checking the DFM operation on the 1GHz range — pressing the F4 button, with no input connected, should give a reading of around 1.2GHz.

Note that the maximum input voltage for reliable counting is 300mV RMS. The input impedance is 560Ω in parallel with 5pF at low frequencies, and 30Ω in parallel with 1.5pF at 1GHz.

Inside the SAB6456 (IC1) is a binary counter which can be set to divide by 64 or 256, depending upon the mode control pin (pin 5). With pin 5 open circuit the division ratio is 64.

What we would really like is a divide-by-10 or divide-by-100 prescaler, but such devices are quite expensive. Instead, we have managed to make do with the divide-by-64 option, followed by an additional divide-by-2 stage implemented with normal ECL circuitry. The fact that our 1GHz signal is divided by 128 instead of 100 does not cause any real problems, as will be shown next month.

As shown in Fig.7, the actual cutoff frequency for the SAB6456 is typically 1.7GHz. After dividing by 128, this leaves a signal of 13MHz for the ICM7216A counter chip. Since typical 7216 devices can count to 15MHz, our DFM can comfortably exceed its nominal 1GHz specification.

The differential outputs of the SAB6456 are at pins 6 and 7 and the output voltage swing is typically from +4V to +5V. The addition of emitter follower stage Q3 to pin 7 gives us normal ECL signals and

PARTS LIST FOR 1GHz DFM

- | | |
|---|--|
| 1 plastic instrument case, 200 x 160 x 70mm (W x D x H) | 1 2N5485 N-channel FET |
| 1 display PCB, code sc041-1187-1, 194 x 61mm | 3 BAW62 high-speed silicon diodes |
| 1 main counter PCB, code sc041-1187-2, 190 x 55mm | 4 1N4001 silicon diodes |
| 1 power supply PCB, code sc041-1187-3, 54 x 44mm | 7 1N914 silicon diodes |
| 1 translucent red acrylic panel, 195 x 64 x 1.5mm | 1 7805 5V 3-terminal regulator |
| 1 Scotchcal label, 195 x 27mm | 8 common anode LED displays, Hewlett-Packard HDSP-5501 or equivalent |
| 1 10MHz parallel AT-cut crystal | 2 red light bar modules, Hewlett-Packard HLMP-2300 |
| 2 BNC panel sockets | 5 miniature red LEDs |
| 8 momentary contact pushbutton switches | 1 red LED (for testing) |
| 1 2155 power transformer | |
| 1 push on/push off SPDT mains switch | Capacitors |
| 1 mains cord and plug | 1 2200 μ F 16VW axial electrolytic |
| 1 cord clamp grommet | 1 1000 μ F 16VW PC electrolytic |
| 1 two-way mains terminal block | 5 10 μ F tantalum |
| 3 solder lugs | 2 0.1 μ F ceramic |
| 2 PC pin connectors | 15 0.01 μ F Philips miniature ceramic plate, type 2222-629 (0.2-inch lead spacing) |
| 2 5mm metal standoffs | 1 0.047 μ F ceramic |
| 3 25mm 6BA screws and nuts | 1 0.022 μ F ceramic |
| 1 7mm dia. plastic plug (as used with mains sockets) | 1 0.0022 μ F ceramic |
| 4 rubber feet | 1 100pF ceramic |
| | 1 39pF NPO ceramic |
| Semiconductors | 1 18pF ceramic |
| 1 SAB6456 prescaler IC (Philips) | 1 4-40pF trimmer capacitor |
| 1 10116 ECL line driver | Resistors (0.25W, 5%) |
| 1 10100 ECL 3-input quad NOR gate | 2 x 10M Ω , 1 x 1M Ω , 1 x 820k Ω , |
| 2 10131 ECL dual D flipflops | 1 x 180k Ω , 2 x 47k Ω , 3 x 10k Ω , |
| 1 ICM7216A 10MHz universal counter | 11 x 4.7k Ω , 3 x 2.2k Ω 1%, 4 x 1k Ω , |
| 1 4024 7-stage binary counter | 15 x 470 Ω , 2 x 270 Ω , 1 x 120 Ω , |
| 4 4016 quad bilateral switches | 4 x 100 Ω , 1 x 33 Ω , 1 x 1k Ω multi-turn trimpot |
| 2 4017 decade counters | Miscellaneous |
| 16 BC549 NPN transistors | Mains rated cable (32cm), hook-up wire (50cm), heatshrink tubing. |
| 1 2N4258 PNP transistor | |

quency to 100MHz), we need to insert a divide-by-10 circuit. This is done in two stages: a divide-by-5 stage consisting of IC5a, IC5b and IC4a, and a divide-by-2 stage consisting of IC4b.

Before we discuss how the divide-by-5 and divide-by-two counters work, note that IC4 and IC5 are dual D flipflops, with two clock inputs per flipflop which are ORed together. Pin 9 is a common clock input for both flipflops, while pins 6 and 11 are separate clock inputs. Either input can be used to clock the flipflop, provided the other is taken to a logic 0, or grounded.

The D flipflops operate as follows: when the clock input goes to a logic 1, the data present at the D input is latched by the flipflop and appears at the Q output.

The divide-by-5 counter

This is a synchronous counter. All three flipflops (IC5b, IC5a and IC4a) are clocked simultaneously from the 100MHz Schmitt trigger output via IC3b. When the counter is not needed, it is stopped by applying a logic 1 to the Reset input (pin 4) of IC4a. However, if F3 is pressed, pin 4 of IC4a goes low and the counter functions again.

The three flipflops are connected to operate as a shift register; ie, each input is connected to the output of the previous flipflop. The input to the first flipflop, however, is connected to the OR of the Q-bar outputs of the last two stages. This gives a count sequence which divides the clock signal by 5.

The divide by two counter (IC4b) is wired with the Q-bar output connected to the D input. This means that each cycle of the clock signal causes the flipflop to toggle and so provide a divide-by-two function. As before, the counter is stopped by applying a logic 1 to its Reset input (pin 13).

Now let us look at the function button logic which involves ten transistors from Q4 to Q14. This part of the circuit controls the signal switching to the ECL-CMOS translator (Q2). Normally, Q4 to Q6 are on while Q7-Q14 are off.

Let's say that function button F1 is pressed (ie, period mode is

these are applied to pin 10 of IC3c which forms part of the signal path control logic.

Control logic


IC3 is a quad NOR gate, type 10100, which selects the appropriate signal routing. Pin 9 of this IC is a common enable input which is grounded, so that IC3a, b, c and d function as 2-input NOR gates.

When button F1 (period) or F2 (frequency to 10MHz) is pressed, pin 13 of IC3d and pin 5 of IC3a go low. IC3a is used as an inverter, so

its output goes high and resets flipflop IC4b. At the same time, IC3d gates the signal from IC2a through to the ECL-CMOS level translator (Q2).

Note that when two ECL gates share a common output pull-down resistor, either or both gates can take the output high, and so an OR function is obtained without using any extra gates. Thus, the ECL-CMOS translator (Q2) can be driven by IC3d when the output of IC4b is low, and by IC4b when IC3d is low.

When button F3 is pressed (fre-

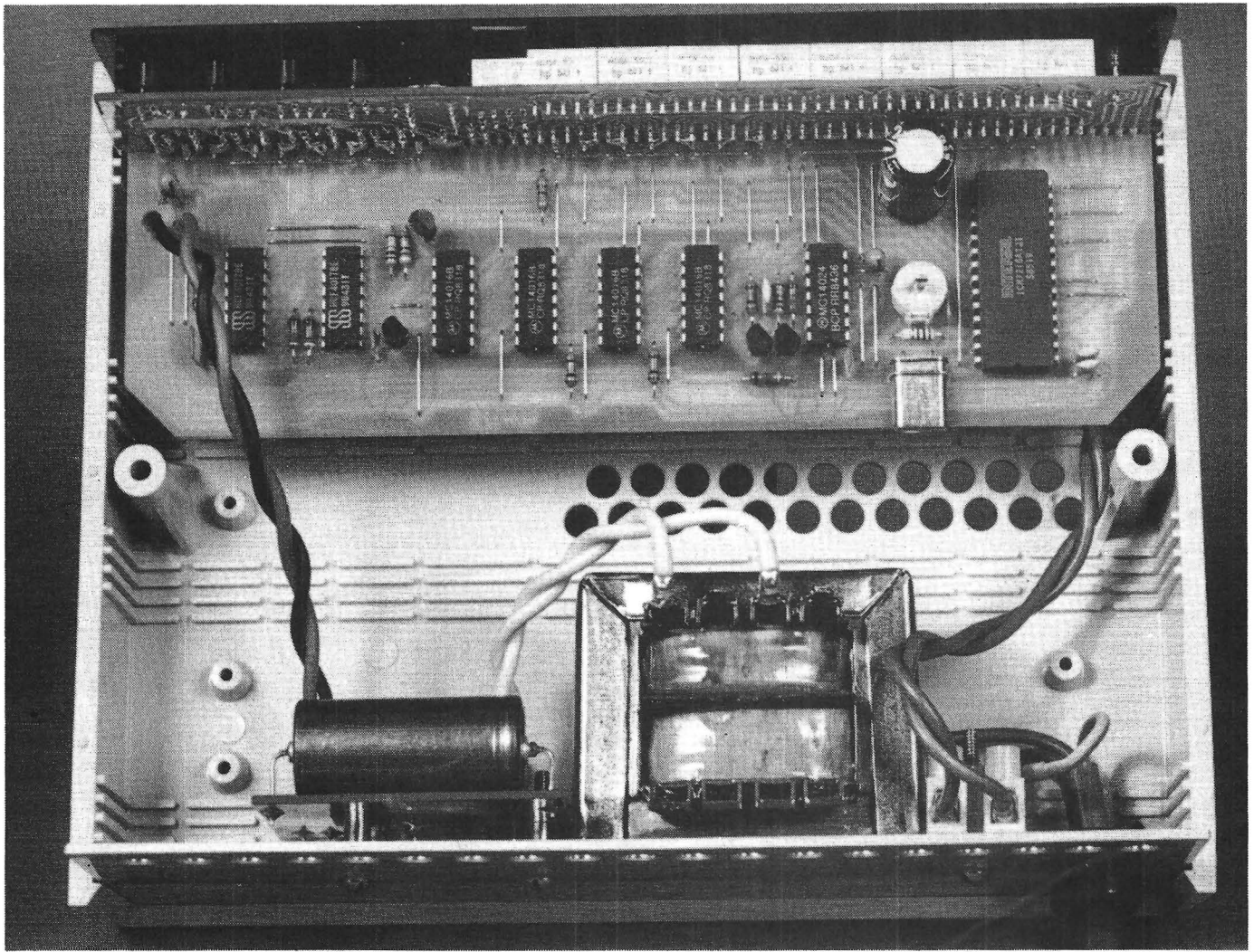

Electronic switching means that internal wiring has been kept to an absolute minimum. Matching slots at the front of the case accept the main PCB and front panel assembly, while power supply components are mounted on the rear panel.

selected). When this happens, the F1 line is latched high by IC13 (4017) and so transistors Q7 and Q8 are turned on. This then turns on LED 4 and LED 2 which are the period mode and μ sec display indicators respectively.

Q8 also controls Q4 via diode D9. Normally, Q4 is turned on by its 4.7k Ω base resistor and pin 13 of IC3d and pin 5 of IC3a are both held high. When F1 is pressed, however, Q8 turns on and pulls Q4's base low via D9. Q4 thus turns off and pin 13 of IC3d and pin 5 of IC3a are pulled low by Q4's 4.7k Ω emitter resistor.

IC3d is now enabled and gates the signal from the 100MHz preamp through to the base of the ECL-CMOS level translator (Q2), as discussed previously.

Note that, during this time, IC4b is held reset by the high on the out-

put (pin 2) of IC3a, while IC4a is held reset by Q5 which is on. Thus, the divide-by-5 and divide-by-2 counters are disabled. Q6 is also on and disables IC3c which controls the signal routing for the 1GHz input.

If F2 (10MHz) is now pressed, Q7 and Q8 turn off and Q9 and Q10 turn on. This turns on LED 5 and LED 3 (via D5) which are the mode and kHz indicators respectively. Q4 is again turned off, this time via D8, and so IC3d again gates through the signal from IC2a to the base of Q2.

If F3 (100MHz) is pressed, Q11 and Q12 are turned on and light LED 6 and LED 3 (via D6). Q12 also turns off Q5 which releases the reset on IC4a and thus enables the divide-by-5 counter. At the same time, pin 2 of IC3a goes low and enables IC4b. As a result, signals

from the 100MHz preamp are now gated via IC3b and pass through the divide-by-5 and divide-by-2 stages before being fed to the ECL-CMOS translator.

Finally, when F4 (1GHz) is pressed, LED 7 and LED 3 light and Q6 is turned off by Q14. Q5 is on and so IC4a will now be disabled. The divide-by-2 counter (IC4b), however, will still be enabled by the low on pin 2 of IC3a. Thus, when F4 is selected, signals from the 1GHz divide-by-64 prescaler are gated by IC3c and fed to the divide-by-2 counter (IC4b).

That's all we have space for this month. When we resume next month, we'll describe the counter circuitry and the latching circuitry for the pushbutton switches. In addition, we'll give you all the construction details.

IT HAD TO HAPPEN!

BUILD-IT-YOURSELF 'AT' COMPUTER!



At last! The perfect opportunity for the hobbyist to build the perfect computer. . . Perfect because it has in it what YOU want! All the features of the "AT" - blinding speed, high expandability, and so on - but you put it together yourself - and \$ave!

There's more: each board or module comes with a full 12 month warranty PLUS individual, professionally prepared manuals - no Jingles to decipher!

And best of all, you don't have to buy it in one hit: add what you want, when you want it (and when the pocket allows it!)

Look at the features:

SUPERB QUALITY HINGED CASE

"Baby AT" case in heavy gauge steel, heavily covered in damage-resistant bone crinkle finish. The lid is hinged and locks up for instant internal access - no more undoing screws! Large enough for expansion - but features a footprint of just 430mm square! Cat X-1005

ONLY \$175

200W POWER SUPPLY

Completely pre-assembled - even to the on/off switch and input sockets! Simply slots into place in cutouts provided in case. Heavily plated steel case for minimum RFI with integral whisper-quiet fan. 200W capacity is ready for . . . anything! Cat X-1010

ONLY \$275

"BABY AT" MOTHERBOARD

Again, completely pre-assembled. No risk of dry joints - you just connect appropriate cables (as described in detailed manual included). On-board capacity for 1Mb RAM and 8 slots for expansion in true "AT" format. Offers 6, 8, 10 & 12MHz speed (switch & software selectable) giving outstanding software compatibility PLUS blinding speed when you need it, and time & date memory with battery back-up. Cat X-1000

JUST \$995

PLUG-IN CARDS

Cards for the various graphic standards, printer ports, serial ports, etc etc. Choose the one that suits your requirements - and remember, you can always upgrade later!

CGA plus Parallel Printer Card Cat X-2010 **\$129**

MGA plus Parallel Printer Card Cat X-8141 **\$149**

EGA Card with Hercules compatibility Cat X-2013 **\$399**

Serial/Parallel/Game Card Cat X-2012 **\$139**

DISK CONTROLLERS

Your choice of hard/floppy or floppy disk controller card: choose the one that suits your needs best. Both plug in to motherboard.

Floppy Controller (2 disk drives 1.2Mb or 360Kb) Cat X-2014 **\$129**

Hard/Floppy Controller (2 of each) Cat X-2008 **\$399**

DISK DRIVES

Also include appropriate cables.

1.2Mb Floppy Disk Drive Cat X-2200 **\$269**

20Mb Hard Disk Drive Cat X-2203 **\$795**


(Other higher capacity Hard Disks available if required)

KEYBOARDS

Two types available:

84 Keys with top quality "Alps" keyswitches Cat X-3820 **\$129.00**

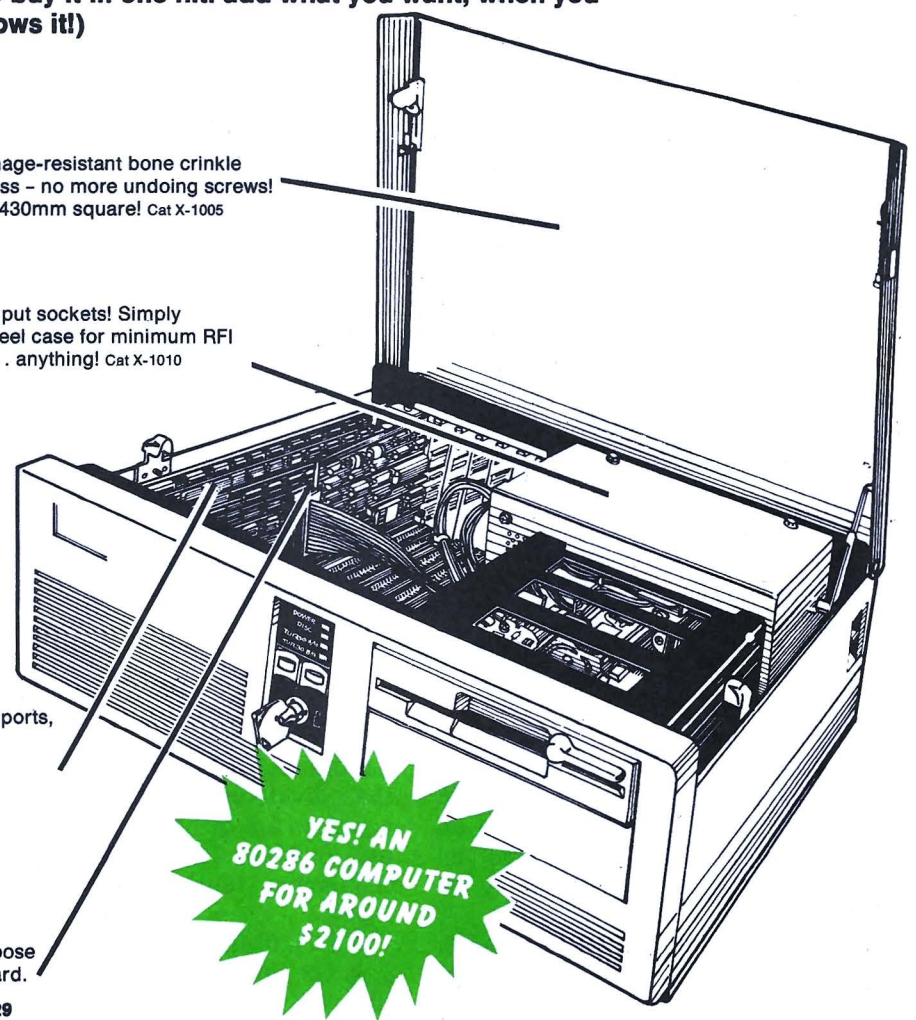101 Keys - with numeric keypad Cat X-3821 **\$149.00**



YES! AN 80286 COMPUTER FOR AROUND \$2100!

WHERE ELSE BUT

DICK SMITH ELECTRONICS

PTY LTD

DSEB450/RT1087

Build (or give!) a Kit this Kitmas...

Kits make great gifts: beats a pair of sox anytime!

Dick Smith's own Fun Way Into Electronics

Here's great value: the Fun Way One gift box. All the components needed to build any of the projects in Fun Way One... and the book is included too! All this for under \$25! Cat K-2605
Projects to build include:
Dog & Cat Communicator
Beer Powered Radio
Morse Code Practice Set
Crystal Sets
Mini Amplifiers And much, much more



\$24.50

Fun Way One Project Packs

Two project packs to allow you to build any of the kits. Project Pack One allows you to build any of the first ten kits in Fun Way One. Project Pack Two gives you the additional components required to build any of the 20 kits (needs Pack one too!) Note - Fun Way One book is NOT included with these kits.

Fun Way One: Project Pack One **\$8.95**
Cat K-2600

Fun Way One: Project Pack Two **\$9.95**
Cat K-2610

Fun Way TWO

Ready for something more advanced? Fun Way Two has another twenty projects to build - all on modern printed circuit boards. And we even teach you how to solder!

Fun Way Two Bonus Pack includes the Fun Way Two book, a quality soldering iron, a pack of solder, a nine volt battery, AND the most popular kit in Fun Way Two: the Wireless Microphone. **\$26.95**
Cat K-2620

Fun Way THREE

The real professionals! Build the Fun Way Three kits and you'll be ready to tackle most projects. The Fun Way Three Bonus Pack includes the Fun Way Three book and not one, but TWO popular Fun Way Three kits: the Cricket and the Mini Amplifier. Great value!
Cat K-2670

\$29.95



One, Two and Three Gift Box

If they're really into electronics, they'll LOVE the gift box. It has kits to build from all three Fun Way books: nearly one hundred dollars value for only \$59.95! Build a flashing brooch, a wireless microphone, cricket, mini amplifier and more. **\$59.95**
Cat K-2680



And the really big one... Get the Jumbo Gift Box!


Over thirty great projects to build from all three Fun Way books. And the books are included! Over \$120 worth of goodies crammed into this value-packed box. Any kid from 6 to 60 would think it was Christmas. (Now that sounds like a good idea!).
Cat K-2690 **\$99.95**

How do you test a Zener?

Let's see. Out with the power supply. Work out the series resistor. Get the voltmeter and put it across the zener. Turn on the supply. Woops! Wrong resistor. One cooked Zener...

Or you can build the Zener Diode Tester. Very simply and accurately checks Zeners without danger. Especially handy in the service lab when the markings are worn off! Cat K-3051

\$29.95

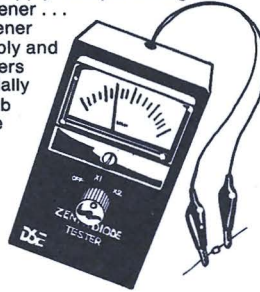

Look Mum. No Bike!


Bikes (the vroom vroom variety) are, unfortunately, very vulnerable. Don't become the victim of a very vulnerable vroom vroom. Fit a bike alarm to your bike and it'll scream its head off if some light fingered larrikin tries to lift it. Easy to build, easy to fit - suits most bikes. Cat K-3249

\$39.95

And one for the Car, Too!


Police statistics are staggering: and your car could be next. Build this simple alarm and the odds are back on your side. It's very easy to make, operates on "voltage drop" principle so no holes are needed for key switches, etc. It works! Cat K-3250

\$16.95

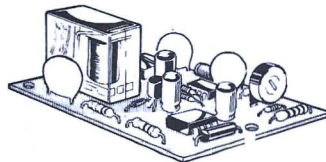

Or the Deluxe Job

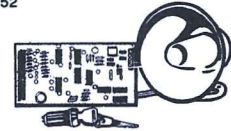The ultimate in protection! One of the best alarms around - better than most commercial units. Includes its own siren output (doesn't rely on car horn), has provision for back-up battery... and it's about the best investment you could make for your car. Cat K-3252




\$79.95

Add an Ignition Killer for 100% Protection


Nothing's worse than a car that misbehaves. Especially if you're trying to knock it off. Imagine. It starts, but very soon splutters and stops. Bill Sykes thinks the car's crook and goes off searching for another! You return to your car, reset the ignition killer - and drive away! Cat K-3255

\$22.95

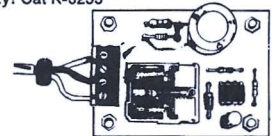

Want a GREAT AMPLIFIER?

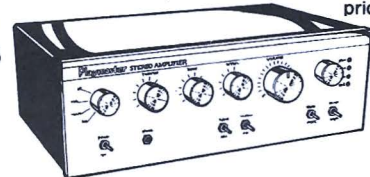Build yourself a MOSFET AMP. It's great! And our value-packed kit makes it even greater! 42 watts per channel into 8 ohms - with professional specs and features. Comprehensive step-by-step manual included to make it easy on you. Compare it to commercial amplifiers at three and four times the price! Cat K-3515




\$219

70cm YAGI KIT

Build your own Yagi for UHF. This 13 element design is simple to construct (all the hard work is done for you!) Strictly while stocks last. Cat K-6305

\$29.95

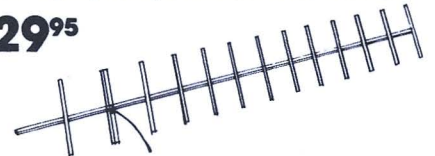

70cm Phasing Harness

Want to stack a couple of Yagis for more gain? Use this ready-made Phasing Harness. At UHF every dB (microBel - as distinct from dB) is a help - so help yourself! Cat K-6299

\$10.95



While stocks last!

DICK SMITH ELECTRONICS

PTY LTD

ORDER BY PHONE: TOLL FREE DSXpress ON (008) 22 6610 For 24 hour despatch

SERVICEMAN'S LOG

With friends like that

“With friends like that, who needs enemies?” So goes the popular saying, implying that someone one trusted as a friend has not come up to scratch in a crisis or, worse, has deliberately betrayed that friendship, usually for his own personal gain. Cynical though the expression may be, there seems to be a lot of it going around.

These thoughts were prompted by a recent experience involving a customer and a video recorder. He was one of my regular customers and the recorder was a model AV14 manufactured by Mitsubishi and marketed by AWA. This is a relatively recent model which first appeared about three years ago, and one with which I am reasonably familiar.

So when the customer opened the conversation with the innocent remark, “Will you have a look at this recorder for me?”, I expected some fairly routine electrical or mechanical fault. “Sure”, I replied, “What seems to be the problem?”

Then he dropped the bombshell: “It’s been dropped”.

That rocked me somewhat. Of all the things one should not do to a video recorder, dropping it would be at the top of the list. Of course there is dropping and dropping — how far had it fallen, on what had it landed, and at what angle? These were questions I wanted to ask, if only to help me assess the likely damage and chances of repair. But the sheepish look on the customer’s face when he made the announcement suggested that such questions might not be diplomatic, at least at this stage.

Picking up the machine, I turned it over and gave it a casual inspection for obvious signs of damage. At first I found nothing, then a closer look revealed a slight flattening of the metal top cover in the rear left hand corner, amounting to only a few millimetres. Well, at least I

could visualise the angle at which it had landed. And with only that much damage externally, maybe the situation wasn’t so bad.

But when I looked through the front loading opening it was a different story. The cassette carrier was at a nasty angle relative to the opening, with the left hand side several millimetres higher than it should have been. That set my imagination racing; I could visualise the main frame being twisted or, more likely, fractured, in which case the machine would be a write-off.

I passed these thoughts on to the customer, and suggested that he leave it with me until I had time to open it up and take a more detailed look. And if the damage wasn’t as drastic as I feared, I could probably give him some idea of what it would cost to fix. And so we left it at that.

A closer look

A few days later, when things were a bit slack, I pulled the top cover off the machine and took a closer look. The mechanical deck is well covered by the main printed

Special Notice

These notes are being contributed by the author who, from 1950 until July of this year, wrote “The Serviceman” in another magazine. We feel sure that regular readers of that series will welcome the opportunity to continue following his electronic adventures in *Silicon Chip*.

circuit board, which would have to be lifted before I could examine the main frame. However, I was agreeably surprised to find that the board itself did not appear to have suffered in any way. I later confirmed that there were no cracks of any kind.


Moving the board clear is a somewhat fiddly job in this model. As well as removing the screws holding the board itself it is necessary to remove the front panel and undo a number of screws which hold the operating controls. These are attached to the main board by flexible leads and some care is needed to ensure that these are not damaged as the board is folded back.

In fact, this part of the exercise was completed without incident, and I was then able to get a good look at the main frame. Strangely enough, the real problem was not immediately obvious. As far as I could see, the frame was neither bent nor cracked and, possibly due to some kind of optical illusion, it took me a few seconds to work out how it was that the cassette carrier was crooked, even though neither it nor the main frame seemed to be damaged.

A frame-up

But suddenly all became clear. The main frame was sitting at an angle, relative to the case, and this was why the cassette carrier did not line up with the front opening. And closer examination revealed just why the frame was at this odd angle.

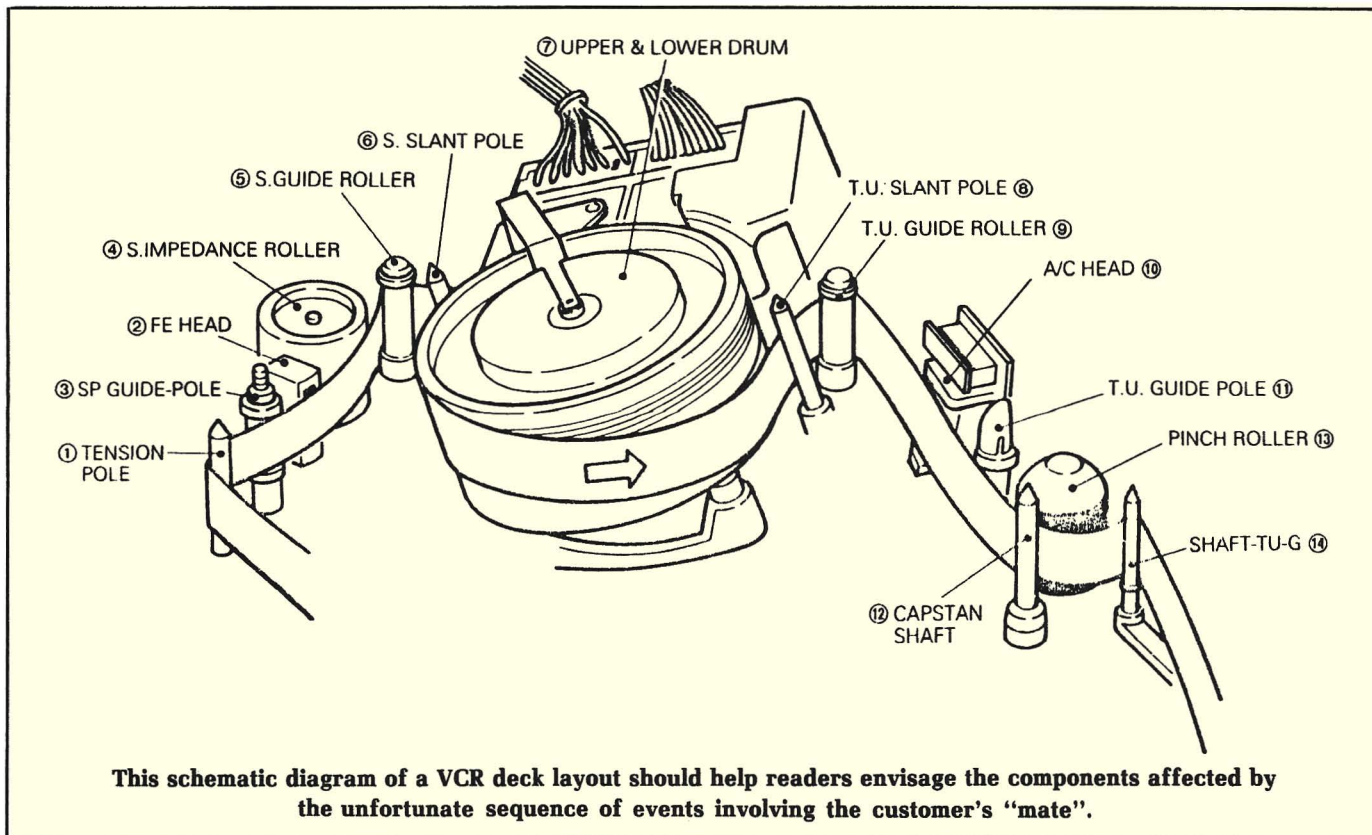The frame is of cast aluminium and is supported in the case by four round pins, or spigots, about 5mm in diameter, which are part of the casting. They are fitted with rubber bushes which, in turn, fit into recesses moulded into the plastic case. And this was where the



damage had occurred.

The spigot near the front left hand corner of the frame had broken off, together with a small piece of the frame, about half the size of a little finger joint. But that was not all; it had wedged itself under the frame in such a way as to lift the left hand corner of the deck, thus creating the odd angle. Such are the weird things that happen when the irresistible force meets the immovable object.

It wasn't much of a job to retrieve the piece of broken casting, whereupon the frame moved back into place and, in spite of the missing support, sat reasonably firm. So normal did everything appear, in fact, that I decided to try loading a cassette. And if it loaded, perhaps it would even play.

So I applied power and, when there was no smoke or other signs of distress, pushed a cassette into the carrier. The carrier accepted it and deposited it on deck in the usual way. Well, so far so good and, thus encouraged, I pressed the play button. For a moment I thought this function was going to work also, but I was disappointed. The two guide rollers — (5) and (9) in the accom-

panying diagram — which normally pick up the tape and wrap it around the drum, moved only a short distance, then jammed.

Finding this fault took a little more time and proved even stranger than what had happened so far. I withdrew the cassette and examined the deck in greater detail. To understand what I found it will be necessary to refer to the accompanying diagram and in particular to the tension pole (1) on the extreme left hand side.

This pole, as its name implies, is used to tension the tape on the supply side of the drum after the two guide rollers have wrapped it around the drum. It is mounted on a small plate, pivoted on a pin and held in place with a circlip, and which has a short rod extending downwards through the deck. This rod is engaged by a lever which exerts the required tension on the tape via the tension pole.

This mechanism sits in close proximity to the curved cut-out in the deck through which the guide rollers, and particularly the supply side guide roller (5) moves during the tape wrapping process. And, by some queer quirk of the forces

generated by the fall, the short downward projecting pin on the plate had been forced out of its own opening and into the guide roller slot, effectively jamming the guide roller.

And while the fact that this had happened at all was puzzling, the real surprise was yet to come. I couldn't believe that this displacement had taken place without some degree of distortion to some of the parts involved, particularly the tension pole plate.

I removed the circlip, pulled the plate out, and examined it carefully. It did not appear to be bent or to have suffered any other form of damage. I replaced it in its correct position, refitted the circlip, then tried the cassette again. And this time it worked; the carrier accepted the cassette, deposited it on the deck and, when I pressed the play button, the two guide rollers picked up the tape, wrapped it around the drum, and set it in motion.

I had connected the machine to a TV set and was gratified to see a picture come up on the screen. Granted, there was evidence of tracking error — not surprising

considering what it had been through — but I felt confident that this would respond to routine adjustment.

So much for complacency

All of which was very encouraging and I felt that I could now regard the machine as repairable and even make a fair estimate as to what it would cost. So much for my complacency. The setup had been running for only a few minutes when the picture suddenly went very snowy, and I had visions of all kinds of nasty faults involving hairline cracks in the main board and the time that might be necessary to track them down.

Fortunately, I made a few simple tests first. I stopped the tape, switched the TV set to an off-air channel, and was rewarded with a snowy picture in that mode also. Further investigation showed that the condition could be created or cured by simply wriggling the plug in the "RF OUT" socket on the recorder. Well, that meant a repair job in that section, but I didn't anticipate that it would be all that difficult.

So it was time to contact the owner, explain the situation, indicate the likely cost of repair, and see what he wanted to do about it. I rang his home number and the phone was answered by his wife. When I explained who I was and that I was calling about the video recorder the reply was a rather flat and slightly aggressive "Oh that".

It didn't need Sherlock Holmes to deduce that there was some lack of domestic agreement in the matter of the video recorder.

Naturally, I wasn't keen to become the meat in any sandwich but, on the other hand, I needed someone to make a decision. But before I could say any more, the lady launched into the story about the recorder, "People seem to take my husband for a soft touch. He bought this recorder in a pub for a

hundred dollars, from one of his mates".

She went on to explain that this mate had been involved in a marital breakup and was short of ready cash. So he had offered my customer "this beaut video recorder for a hundred dollars".

Of course, he had conveniently forgotten to mention anything about the recorder's unfortunate encounter with a hard floor, and so the deal was struck, my customer believing that he had acquired a real bargain. It was only when he brought the machine home and tried to use it that he found it wouldn't even accept a cassette. Exactly how he eventually learned what had happened to the machine was not revealed. Perhaps he tackled his mate; perhaps he heard it from somebody else. But one thing is certain: with friends like that, who needs enemies?

So much for history

So much then for the history. What about the present? I explained to the lady that her husband may not have done so badly after all. I felt sure that the recorder could be repaired, with a possible outlay between \$150 and \$200, with the latter figure as a firm upper limit. This meant that they would get a recorder for between \$250 and \$300 — a bargain by any standards.

As a bonus, there was the fact


that the machine was a current model and, based on my examination of it, one that had had very little use. In that sense it was almost brand new.

Apparently I was a better salesman than I realised because, by the time I finished, the lady gave me the go-ahead to fix the machine, without waiting to discuss it with her husband. (Curse my fatal charm).

But now I had to deliver the goods. The most important job was to somehow refit the spigot to ensure that the deck would remain stable. Fortunately, the nature of the break made this easier than it might otherwise have been. First, there was the fact that the spigot had not broken off cleanly but had taken a piece of the main frame with it. And second, the angle of the break was such that such stress as it would normally encounter would, if anything, tend to press the two pieces of metal together, rather than the reverse.

There was also the fact that, dropping aside, there is not a great

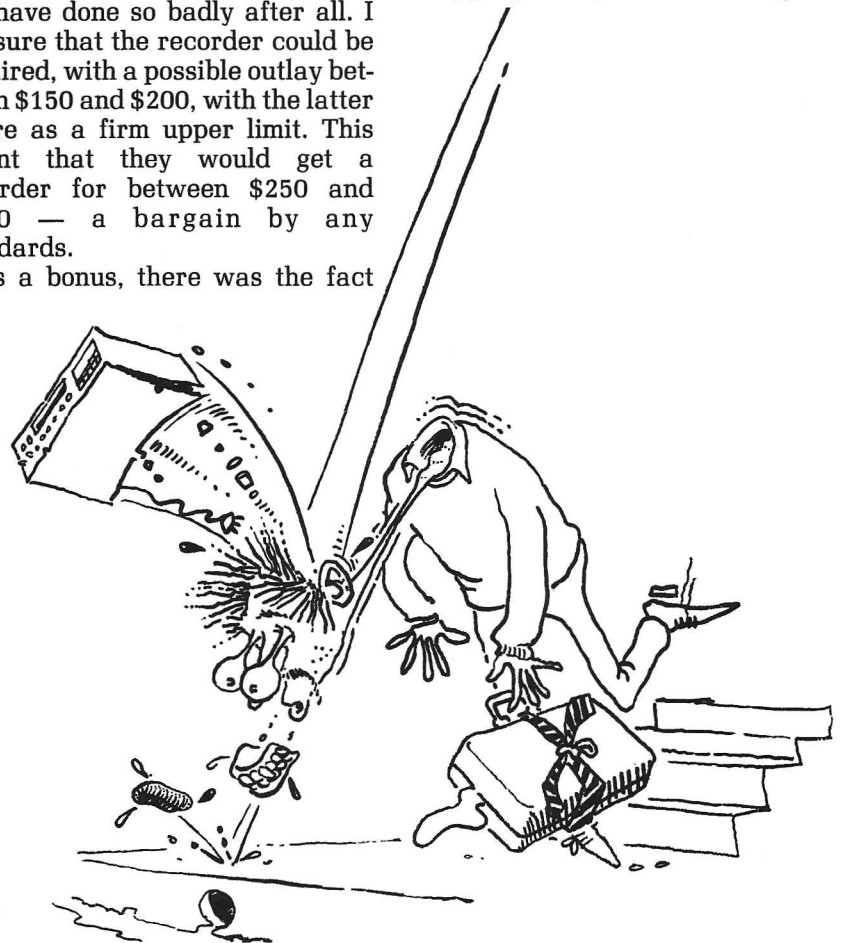THE VIDEO HAD BEEN INVOLVED IN A MARITAL BREAK UP.....



deal of stress on these spigots; they merely support the weight of the deck. Taking all these factors into account, the repair I envisaged was somewhat unorthodox but, I felt, quite practical. It was based on an epoxy mixture called "Plasti-Bond"; a product which, if mixed correctly, cures to a rock hard finish.


So I mixed up a batch, coated the two mating surfaces to provide an adhesive function, pressed them together, then built up a thick coating around the joint, taking advantage of as many irregular contours of the frame as possible to provide the best possible grip. The result was a substantial block of epoxy around the joint which should withstand any reasonable stress it is likely to encounter.

The next thing to be tackled was the fault involving the "RF OUT" socket. This socket is mounted on a metal box which contains the splitter amplifier and getting at this is quite a job. It is closely linked to the tuner as well as the main board and a lot of leads have to be undone, many needing the solder sucker, before the box can be withdrawn far enough to work on it. Then the soldering iron is needed to open the box because the lid is soldered on.

I eventually gained access to the inside of the box and the rear of the socket. The pin from the socket protrudes through a hole in a printed circuit board and is soldered to a narrow copper pattern surrounding the hole. The hole is rather larger than the pin, the solder forming a bridge across the gap.

This arrangement doesn't impress me very much because even normal plugging and unplugging likely to be encountered in typical use must tend to move the pin slightly, putting a stress on the soldered joint and copper pattern. In this case there had been an abnormal stress on it because the body of the socket was bent several degrees relative to its mounting lugs, and the copper pattern had been pulled away from the board and broken, although making intermittent contact.

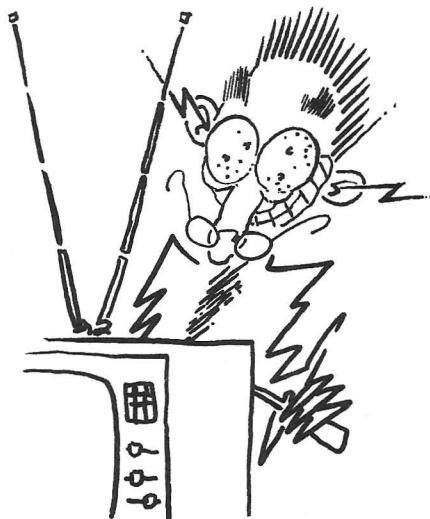I removed the socket, straightened it, then refitted it. I ran some solder around the pin in an effort to



**..SUPPOSED TO RUN
AT 15V, BUT WAS, IN
FACT, CLOSER TO
100V ~ ~ ~ ~**

fill up the hole in the board and provide mechanical rigidity, then replaced the missing copper pattern with a short length of fine wire. I reasoned that if there was any movement by the pin, the wire should be flexible enough to cope with it.

Looking at the damage to the socket etc, I evolved a theory as to how it had come about. I suspect that the lead from the "RF OUT" socket to the TV set was rather short and, when the recorder fell, this lead took most of the weight, even if it wasn't short enough to prevent one corner of the machine hitting the floor.

We'll never know for sure, of course, but something had certainly put a lot of stress on that socket. And it had also contributed a lot to the cost of the repair, due to the difficulty of getting at the fault.

Only the tracking now remained to be adjusted and this was a fairly routine job. When it was finished, the recorder turned in a first class performance and I had no qualms about have advised the owner to let me go ahead with it. The final bill came out about midway between the figure I had quoted and the owner paid up quite happily.

All that was several weeks ago, but the owner was in the shop a few days ago on another matter and confirmed that the recorder is per-

forming beautifully and had been given "a bit of a flogging". I also gained the impression that any initial reservations on the part of his good lady, concerning his "bargain", had long since been dispelled.

So I not only saved a recorder; I might have saved a marriage as well!

A fallen General

My next story is on a quite different theme although some aspects of it are just as puzzling. It concerns a General GC-181 48cm colour TV set, one of several belonging to a local motel and used in the guests' apartments. And the initial description from the owner was simple enough; no picture and no sound.

This description was confirmed when I finally switched the set on in the workshop; there was no sound — and neither was there any picture for the very good reason that we had a classic case of frame collapse. Initially, I couldn't decide whether this was likely to be two separate faults, or whether there was a common factor, such as a supply rail, which could be responsible for both.

But before trying to track the faults on a logical basis I decided to give the set a routine check, dictated by long experience. This set consists of a chassis and main board mounted horizontally in the bottom of the cabinet, plus several auxiliary boards mounted vertically on the main boards by means of plugs and sockets. Among these are the IF Board, Vertical/Power Board, Audio/Horizontal Board etc, plus a Neck Board on the tube.

Most of the plugs and sockets are 6-pin types, some boards using two or more such devices to provide the necessary connections. The setup is a very convenient one for servicing, but has not been without problems of its own. The plugs, or male connectors, are mounted on the main board and the sockets on the auxiliary boards, and connections between these are prone to failure.

It is the plugs on the main board which are the main offenders. The pins pass through the board and are soldered to the copper pattern on the underside, and it is here that

faulty joints are frequently encountered. As a result, I have long since made it a practice to tackle these joints as a matter of routine whenever I encounter one of these sets, regardless of the fault. And it is surprising how often nothing more is needed to fix the fault.

This procedure is further encouraged by the fact that the underside of the main board is fairly easy to get at. Undoing three screws will release the main chassis and allow it to be pulled back far enough in the cabinet to reveal most of the main board underside. And, being a relatively small set, it is easy to tip the cabinet on its side to make it easy to work on.


Having done this, and prompted by the frame collapse, I naturally looked first to the two plugs which feed the vertical board. And there it was; around one of the pins (pin 12 of P403) was a tiny patch of what looked like green corrosion. The green lacquer on these boards made it difficult for me to be certain until I checked with a jeweller's loupe, but then there was no doubt.

But there was something strange about the condition. For one thing, it appeared to be quite small and confined to this one spot. And even stranger, the corrosion was quite wet. Now I have encountered dry joints, fractured joints, and many kinds of faulty joints, but this is the first time that I have found a wet joint. But there it was, and I can offer no logical explanation for it. I checked carefully for evidence of spillage of any kind around the cabinet or anywhere inside the set, but there was not the slightest sign.

So I set to repair the damage. Having cleared away the corrosion I soldered a short length of tinned copper wire to the pin and then soldered this to the copper pattern some little distance away, where it should bypass any long term corrosive effects on the copper track. Then I switched on the set and tried again.

Still no sound

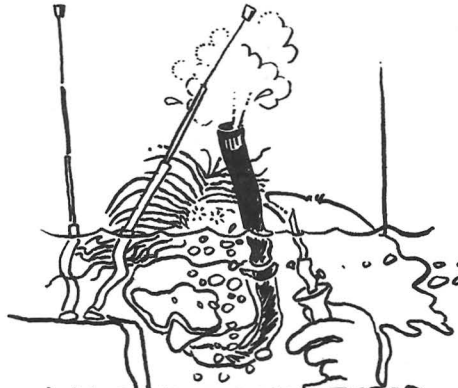It came good, at least in that I had a picture. But there was still no sound. So it appeared that there were two separate faults. I pulled



NOW, I HAVE ENCOUNTERED DRY JOINTS, FRACTURED JOINTS, AND MANY KINDS OF FAULTY JOINTS, BUT THIS IS THE FIRST TIME THAT I HAVE FOUND A WET JOINT

out the audio/horizontal board, which, as its name implies, carries the audio output stage and horizontal oscillator stage, and reconnected it via extension leads, of which I have several for this set. Then I reached for the voltmeter for a routine check.

I didn't get far. The supply rail for the audio stages is supposed to run at 15V but was, in fact, closer to 100V. Just where this was coming from I had no idea initially, but I didn't like the chances that the three transistors involved — the two output transistors and the driver — had survived the situation.

It was the physical location of the audio board that gave me the clue. It sits alongside the vertical board which had suffered the faulty plug connection. More importantly, this plug is directly alongside the plug for the audio board, and pin 12 of the latter which carries the 15V supply is alongside pin 12 for the vertical board, which sits at around 106V. What's more, the two copper tracks run side by side for some distance.

And that's where the trouble was. Whatever the moisture was that had corroded the joint had also apparently penetrated the board and created a path between the two tracks. It is not the first time I have encountered such leakage problems and I have developed a treatment

which has proved very effective in the past.

The idea is to dig a trough between the two tracks. I use a very small drill, driven by a variable speed power drill, and used as a simple router. It requires a little skill but is not all that difficult if one takes one's time. I took about 15 minutes to do this job but, at the end of that time, all signs of the spurious voltage had vanished. I finished it off with a spray of CRC Clear Urethane Seal Coat, 02049, which is available in an aerosol pack.

Then I turned my attention to the audio board and the transistors. As it turned out, only the two output transistors, TR952 and 953, had been damaged and, interestingly enough, one of them had gone open circuit. This was fortunate because, otherwise, the spurious voltage would not have been so immediately apparent. Y'gotta win sometimes!

Anyway, that was it. Two new transistors put the sound section back into action and, after a routine check-up, the set was returned to its owner. But I'm still puzzled about the corrosion and what caused it. And why was it so isolated?

We'll never know

We'll never know I suppose, but here is one other interesting point. My regular readers will recall that several years ago — September 1983 to be exact — I told a story about a set from a motel, a Precedent GC-181 (no relative of the General GC-181), in which severe corrosion was the major problem. In that case, the corrosion was almost certainly caused by the previous proprietor attempting to repair some soldered joints using spirits of salts as a flux.


Well, this latest case came from the same motel. Was this another legacy from our heavy-handed plumber-cum-serviceman, but one which had lain dormant for all these years? I agree that the time factor is against this theory, unless the degree of pollution was extremely slight, and it took all these years and perhaps some excessive humidity to provide the final straw.

So what do you think?

BOOKSHELF

Be the boss of DOS

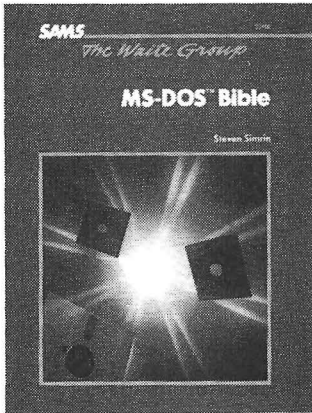MS-DOS BIBLE, by Steven Simrin. Published 1985 by Howard W. Sams, Inc Indianapolis, Indiana. Soft covers, 190 x 248mm, 385 pages. ISBN 0 672 22408 9. Price \$39.95.



Anyone who buys an IBM PC or PC-compatible immediately comes up against the mysteries of DOS which stands for Disc Operating System. IBM PCs use PC-DOS while compatibles use MS-DOS but both are virtually identical since they were created by the same company, Microsoft.

Some DOS manuals are positively labyrinthine in their approach while others are quite good. Ultimately, the hard road of experience is the only way to become proficient at using DOS commands but you can be helped along considerably by a well-written book on the subject. And even if you are quite proficient at using DOS and may be using it for quite advanced programming, a reference book on DOS can still be very useful.

Such a book is the *MS-DOS Bible*, written by Steven Simrin.

The *MS-DOS Bible* assumes no prior knowledge on the part of the reader. The only assumption it makes is that you have just purchased or have otherwise gained access to a PC and want to know how to turn it on. Most people buying a PC will also have a specific purpose for which they have purchased software and therefore

their initial involvement with DOS will be as minimal as possible. As time goes on though, you need DOS more and more if you are to fully utilise the power of your computer.

At *Silicon Chip* we found ourselves in just this situation when we began setting up our computers to cope with the task of preparing and editing copy, and transmitting it via modem to the typesetters.

We found *MS-DOS Bible* quite helpful as we created batch files, disc directories, installed hard disc drives and otherwise readied the systems for work.

There are twelve chapters in all, plus a number of appendices.

Some of the chapter headings are as follows: MS-DOS Files, Directories, Paths and Trees, Installing a Fixed Disc, MS-DOS Batch Files, Redirection, Filters and Pipes, EDLIN, the MS-DOS Text Editor and Structure of MS-DOS.

As with MS-DOS itself, you only need to use as much of the book as is required for the task of the moment. It makes a very good reference. Highly recommended. Our sample copy came from Jaycar Electronics.

Logic made clear

Understanding Digital Logic Circuits, by Robert G. Middleton. Published 1982 by Howard W. Sams Inc, Indianapolis, Indiana. Soft covers, 136 x 215mm, 392 pages, copiously illustrated with diagrams. ISBN 0 672 21867 4. Price \$34.95.


For people who have grown up with the analog side of electronic circuitry, the transition to digital logic can be difficult. There is such a large range of new devices to learn about and the different logic families are not compatible.

There is one consolation that we can offer to anyone who is presently making that transition: when you finally do become familiar with logic circuitry, there is less to it than meets the eye. Certainly, it is not as complex as the great range of analog circuitry.

Now we have just come across an ideal book to teach yourself about logic circuits. Entitled "*Understanding Digital Logic Circuits*" by Robert G. Middleton, it is written specifically for service technicians. They are now having to repair some of the more exotic equipment such as radio scanners, two-way radios, pushbutton TV tuners, VCRs and so on, all of which contain more and more logic circuitry.

While the book is written with technicians specifically in mind, anyone who has a smattering of electronics will find it easy to follow. It starts off with two chapters on gates which are really worthwhile. If you fully absorb all that is in those two chapters, including the material on negated (or reverse) logic, you will be well up on the subject.

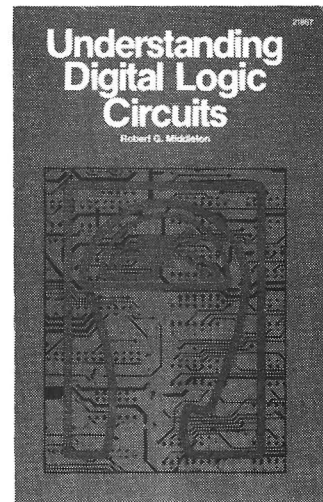We won't bother to give a full description of the 19 chapters but



suffice to say that the subject of logic circuitry is very well covered with a practical approach throughout. There are chapters on Adders, Flipflops, Registers, Counters, Encoders and Decoders, Parity Generators and Checkers, Multiplexers and Demultiplexers, Memories, Digital Voltmeters and Transmission Lines.

We can highly recommend this text. It is one of the best we have come across and is available from Jaycar Electronics. 