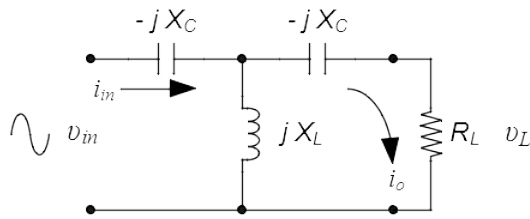


Constant Alternating Current Source



$$Z_{in} = -jX_c + \frac{jX_L(R - jX_C)}{jX_L + (R - jX_C)}$$

Let $X_C = X_L = X$

$$Z_{in} = \frac{X^2}{R}$$

$$i_{in} = \frac{v_{in}}{Z_{in}} = \frac{v_{in}R}{X^2}$$

$$i_o = i_{in} \frac{jX}{R}$$

$$i_o = \frac{jv_{in}}{X}$$

This shows that the output current is independent of the value of load resistance. Load voltage v_L leads input voltage by 90° .

$$X_C = \frac{1}{\omega C} \quad X_L = \omega L$$

For $X_C = X_L = X$

$$\frac{1}{\omega C} = \omega L$$


$$\omega^2 = \frac{1}{LC}$$

$$\omega = \sqrt{\frac{1}{LC}} \text{ r/s}$$

$$f = \frac{\omega}{2\pi} \text{ Hertz}$$

$$X = L\sqrt{\frac{1}{LC}}$$

$$X = \sqrt{\frac{L}{C}} \text{ ohm}$$

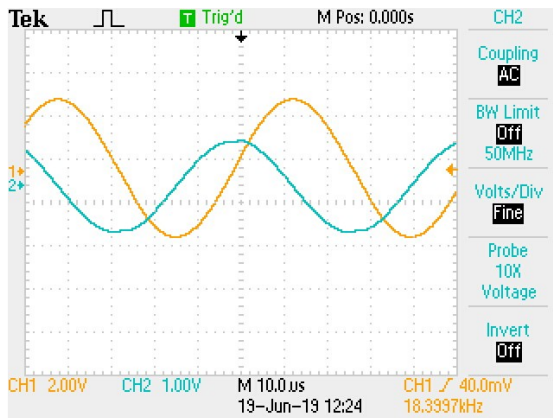


Test 1

Load resistor 50Ω

Load voltage about 2V peak-to-peak

Measured $v_L = 0.384V$

Calculated $i_L = 7.68mA$

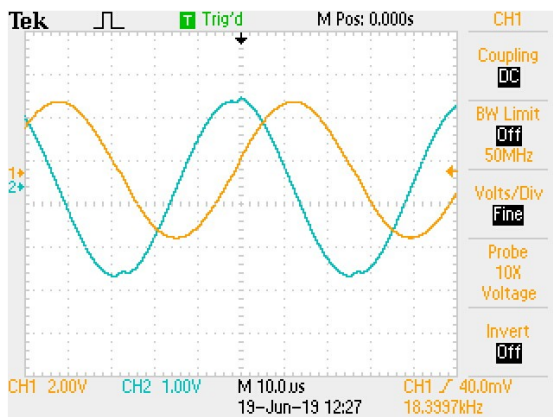


Test 2

Load resistor 100Ω

Load voltage about 4V peak-to-peak

Measured $v_L = 0.773V$

Calculated $i_L = 7.73mA$

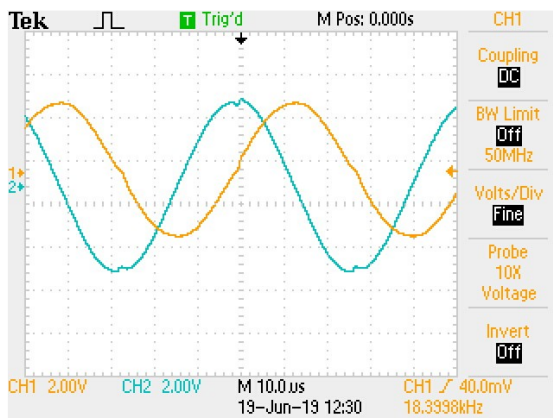


Test 3

Load resistor 200Ω

Load voltage about 8V peak-to-peak

Measured $v_L = 1.495V$

Calculated $i_L = 7.475mA$

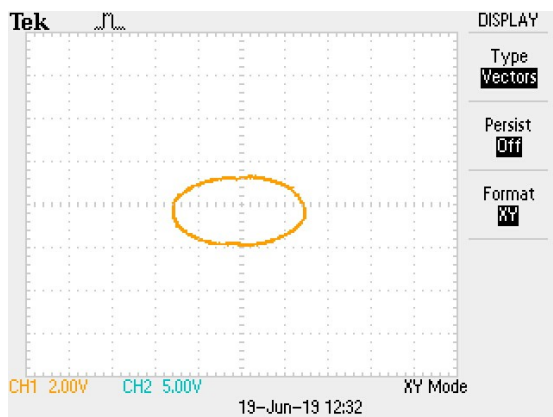

Test 4


Load resistor 100Ω

X/Y plot (ch1 X axis, ch2 Y axis)

This Lissajous pattern shows that input and load voltages are at 90° to each other, as expected from the theory.


Appendix A

Constant Current Design Graphs

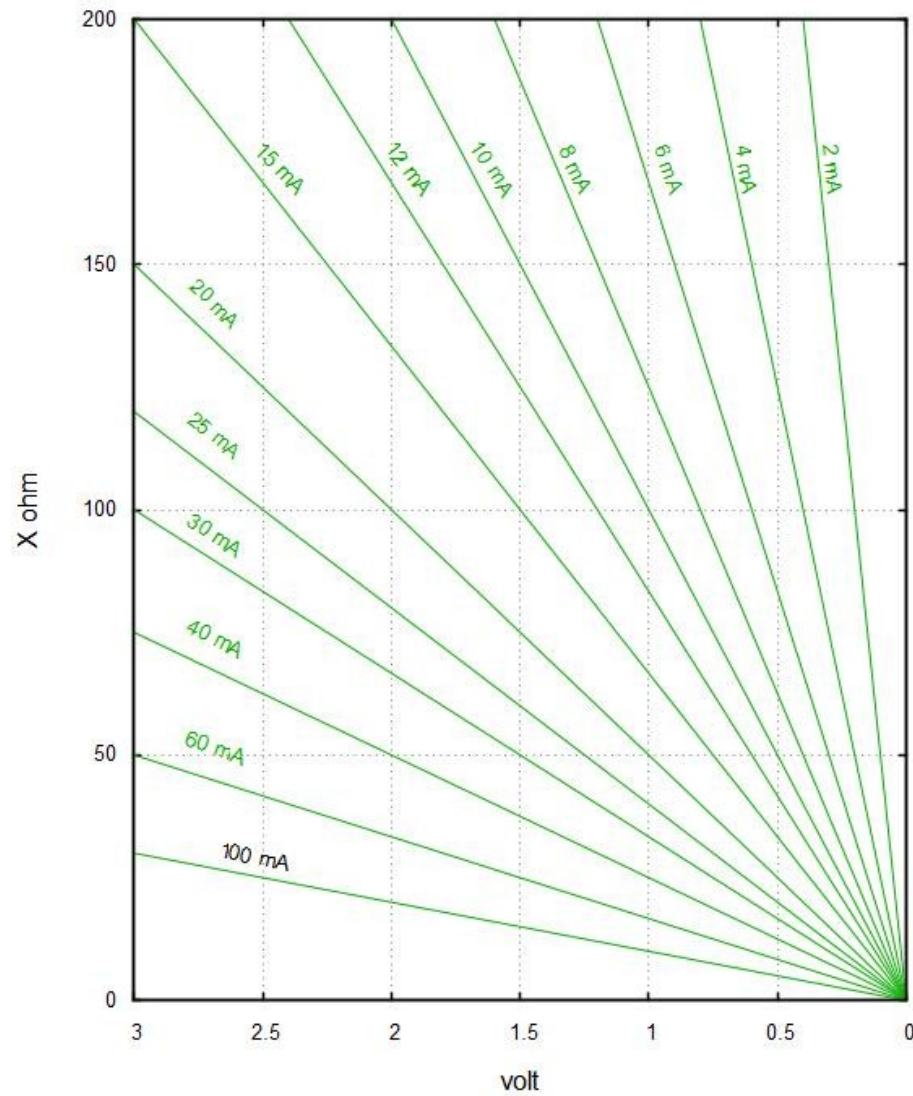

Impedance X ohms and the driving *voltage* determine the RMS value of the current.

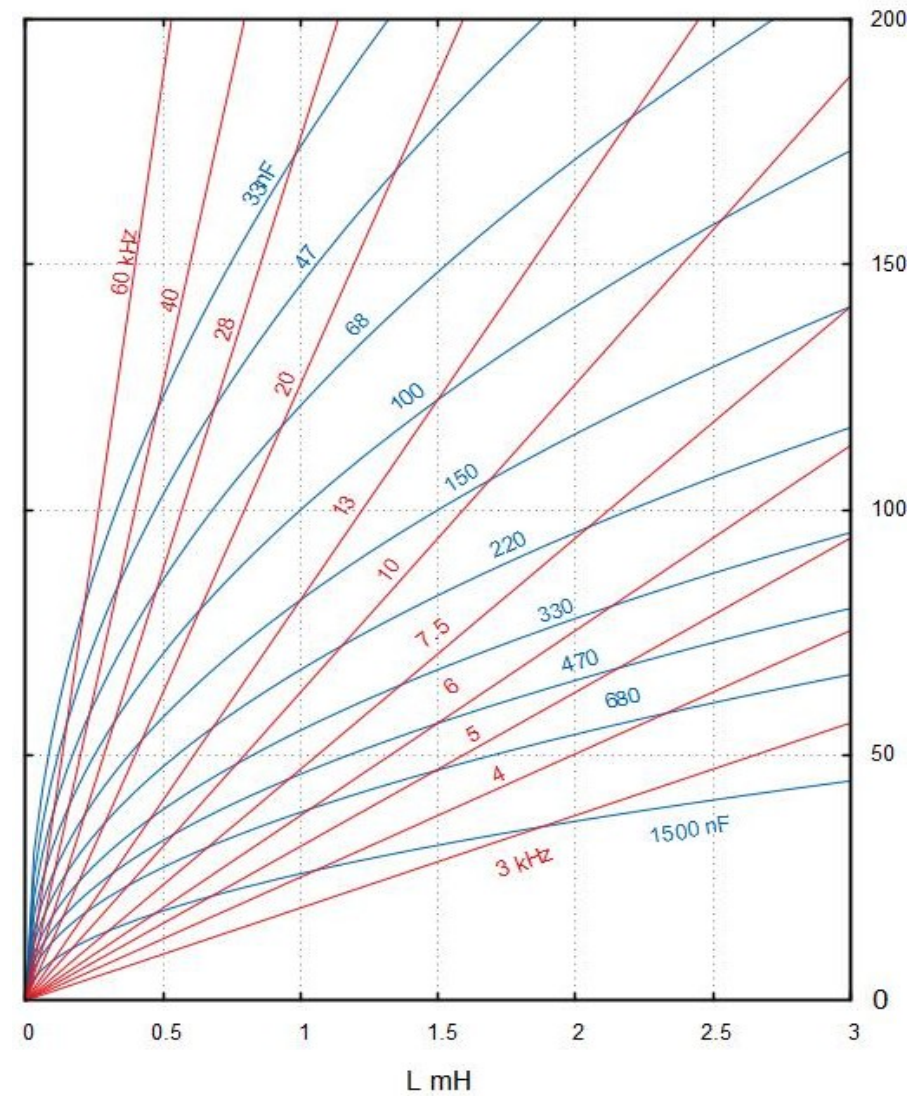gnuplot software was used to generate these graphs (www.gnuplotting.org)



Circuit components L and C determine impedance X ohms and the *frequency* of the input signal.